

ECE 3401

Lecture 2

Digital Design Fundamentals

Digital Design Fundamentals


- **Combinational circuit basics**
 - Basic operators
 - Boolean algebra
 - Complex gates
 - Logic minimization

- **Sequential circuit basics**
 - Latches and flip-flops
 - Finite state machines

Basic Operators

- AND


$$f(A,B) = A \cdot B = A \cap B$$

 

A	B	A·B
0	0	0
0	1	0
1	0	0
1	1	1

- NAND
 
$$f(A,B) = \overline{A \cdot B} = \overline{A \cap B}$$



A	B	$\overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0

- OR

$$f(A,B) = A + B = A \cup B$$



A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

- NOR

$$f(A,B) = \overline{A + B} = \overline{A \cup B}$$



A	B	$\overline{A + B}$
0	0	1
0	1	0
1	0	0
1	1	0

Boolean Algebra

- Unity operators

$$A + 0 = A$$

$$A \cdot 1 = A$$
- Complement

$$A + \overline{A} = 1$$

$$A \cdot \overline{A} = 0$$
- Commutativity

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$
- Associativity

$$A + (B + C) = (A + B) + C$$

$$A \cdot (BC) = (AB) \cdot C$$
- Distributed Law

$$A \cdot (B + C) = AB + AC$$

$$A + BC = (A + B) \cdot (A + C)$$

Boolean Algebra

- Duality $f(A,B,1,0,+, \cdot) = \overline{f(\overline{A}, \overline{B}, 0, 1, +, \cdot)}$

$$A + A = A \qquad A \cdot A = A$$





$$1 + A = 1 \qquad 0 \cdot A = 0$$

$$A + AB = A \qquad A \cdot (A + B) = A$$

$$A + \overline{A}B = A + B \qquad A \cdot (\overline{A} + B) = A \cdot B$$
- DeMorgan's Theorem

$$\overline{A + B} = \overline{A} \overline{B}$$
    
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



Complex Gates

- Exclusive OR (XOR)/Exclusive NOR (XNOR)

$$X \oplus Y = X \overline{Y} + \overline{X} Y \qquad \overline{X \oplus Y} = X Y + \overline{X} \overline{Y}$$



- Uses for the XOR and XNOR gate include:
 - Adders/subtractors/multipliers
 - Counters/incrementers/decrementers
 - Parity generators/checkers


X	Y	$X \oplus Y$
0	0	0
0	1	1
1	0	1
1	1	0

- The XOR function may be implemented
 - directly as an electronic circuit (truly a gate)
 - interconnecting other gate types (used as a convenient representation)

Odd/Even Function

- The XOR function of ≥ 3 variables is called an *odd function* or *modulo 2 sum (Mod 2 sum)*
 
$$X \oplus Y \oplus Z = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$



$$X \oplus 0 = X$$

$$X \oplus 1 = \bar{X}$$

$$X \oplus X = 0$$


$$X \oplus \bar{X} = 1$$

$$X \oplus Y = Y \oplus X$$

$$(X \oplus Y) \oplus Z = X \oplus (Y \oplus Z) = X \oplus Y \oplus Z$$


- The XNOR function of >3 variables is the *even function*

Parity Generators and Checkers

 


 - Example: $n = 3$

- Generate a parity code word of length 4 with odd parity generator
- Check the parity code word of length 4 with odd parity checker:



 
- $P = X \oplus Y \oplus Z$, $E = X \oplus Y \oplus Z \oplus P$




- If Y changes during transmission (between generator and checker), then $E = 1$ indicates an error.

Buffer

 - A buffer is a gate with the function $F = X$:



 - In terms of Boolean function, a buffer is the same as a connection!
- So why use it?
 - A buffer is an electronic amplifier used to improve circuit voltage levels and increase the speed of circuit operation.



Hi-Impedance Outputs

- Logic gates introduced thus far
 - have 1 and 0 output values
 - cannot have their outputs connected together
 - transmit signals on connections in only one direction
- Three-state logic adds a third logic value: Hi-Impedance (Hi-Z)
- The presence of a Hi-Z state makes a gate output as described above behave quite differently:
 - “1 and 0” → “1, 0, and Hi-Z”
 - “cannot” → “can”
 - “only one” → “two”


Hi-Impedance Outputs (Contd.)

- The Hi-Z value behaves as an open circuit
 - looking back into the circuit, the output appears to be disconnected
- Hi-Z may appear on the output of any gate, but we restrict to gates:
 - a 3-state buffer
 - a transmission gateeach of which has one data input and one control input

The 3-State Buffer

- For $EN = 0$, the OUT is Hi-Z regardless of the value on IN

Symbol

 


- For $EN = 1$, the OUT follows the input value

Truth Table

EN	IN	OUT
0	X	Hi-Z
1	0	0
1	1	1

Transmission Gates

 
- The transmission gate is an electronic switch for connecting and disconnecting two points in a circuit
 - $C = 1, Y = X$ ($X = 0$ or 1)
 - $C = 0, Y = \text{Hi-Z}$



- Since X and Y as input and output are interchangeable, and signals can pass in both directions

More Complex Gates

 - SOP or POS structures with and without an output inverter.
 - SOP: $F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$
 - POS: $F = (A + B + C) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C})$
- Naming:
 - A – AND, O – OR, I – Inverter
 - Numbers of inputs on first-level “gates” or directly to second-level “gates” – AOI 221



- These gate types are used because:
 - The number of transistors needed is fewer than required by connecting together primitive gates
 - Potentially, the circuit delay is smaller, increasing the circuit operating speed

Logic Minimization

- Minimizing SOP representation to MSP
- Using Karnaugh Map

$$F = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \overline{A}BC + ABC\overline{C}$$

$C \backslash AB$	00	01	11	10
0	0	1	1	1
1	1	0	0	1

$F = B\overline{C} + \overline{A}B + \overline{B}C$

K-Map Example

$AB \backslash CD$	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

(a) Location of minterms

$AB \backslash CD$	00	01	11	10
00	1	0	0	1
01	0	1	0	0
11	1	1	X	1
10	1	1	X	1

Four corner terms combine to give $B'D'$

$A'BD$

$$F = \sum m(0, 2, 3, 5, 6, 7, 8, 10, 11) + \sum d(14, 15)$$

$$= C + B'D' + A'BD$$

(b) Looping terms

Logic Minimization


- Minimizing POS representation to MPS
- Using Karnaugh Map

$$F = (A + B + C) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C})$$


$C \backslash AB$	00	01	11	10
0	0	1	1	1
1	1	0	0	1

$$F = (A + B + C) \cdot (\bar{B} + \bar{C})$$

D-Latch

 

D latch

 

“Latch” is an important notion: its input is controlled by a gate input C, when C goes from high to low, the state of the device holds.

D flip-flop

- Rising edge triggered D FF
- Timing parameters:
 - Setup time t_{su} : input must be stable before the clock edge
 - Hold time t_h : input must stay stable after the clock edge
 - Clock to Q t_{c-q} : maximum time for output to be stable after the clock edge

