

## ***ECE 3401 Lecture 5***

---

### ***Basic VHDL Modeling***

## **VHDL Structural Elements**

---

- **Entity:** description of **interface** consisting of the port list.
  - The primary hardware abstraction in VHDL, analogous to a symbol in a block diagram.
- **Architecture:** description of the **function** of the corresponding module.
- **Process:** allows for a **sequential** execution of the assignments
- **Configuration:** used for simulation purposes.
- **Package:** holds the definition of commonly used data types, constants and subprograms.
- **Library:** the logical name of a collection of compiled VHDL units (object code).
  - Mapped by the simulation or synthesis tools.

## Data Objects

---

- Data objects hold a value of specified type. They belong to one of three classes:
  - Constants
  - Signals
  - Variables
- **Constants** and **variables** are typically used to *model the behavior of the circuit*.
- **Signals** are typically used to *model wires and flip-flops*
- Must be declared before they are used

## Constants

---

- A constant holds a value that cannot be changed within the design description.
- **Constant** must be declared in *Entity, Architecture, Process, Package*.
  - A constant defined in a **package** can be referenced by any entity or architecture for which the package is used.
  - **Local Property:** A constant declared in an **entity/architecture/process** is visible only within the local environment
- **Example:**
  - **constant** RISE\_TIME: TIME := 10 ns;  
-- declares a constant RISE\_TIME of type TIME, with a value of 10 ns
  - **constant** BUS\_WIDTH: INTEGER := 8;  
-- declares a constant BUS\_WIDTH of type INTEGER with a value of 8.

## Constants

---

ENTITY example IS

**CONSTANT** width : integer :=8;

    PORT ( input : IN bit\_vector (width-1 DOWNT0 0);  
          output: OUT bit\_vector (width-1 DOWNT0 0);

END example;

- The above constant represents the width of a register.
- The identifier **width** is used at several points in the code. To change the width requires only that the constant declaration be changed and the code recompiled.

## Signals

---

- **Signal** represents the **logic signals** or **wires** in a circuit. Signals can also represent the **state of a memory**
- There are three places in which signals can be declared in a VHDL code
  - Entity declaration
  - Declarative part of an architecture
  - Declarative part of a package.

## Signals

---

- A signal has to be declared with an associated **type**:
  - SIGNAL signal\_name : type\_name;
- The signal's type\_name determines the legal values that the signal can have and its legal use in VHDL code.
- **Signal types:**
  - (1) bit (2) bit\_vector (3) std\_logic
  - (4) std\_logic\_vector (5) std\_ulogic
  - (6) signed (7) unsigned (8) integer
  - (9) enumeration (10) boolean

## Signal – Example (1)

---

- SIGNAL Ain : BIT\_VECTOR (1 TO 4);
- Note:
  - The syntax “lowest\_index TO highest\_index” is useful for a multi-bit signal that is simply an array of bits.
  - In the signal Ain, the most-significant (left-most) bit is referenced using lowest\_index, and the least-significant (right-most) bit referenced using highest index.
- Example:
  - The signal "Ain" comprises 4 bit objects.
  - The assignment statement Ain <= "1010"  
Results in Ain(1) = 1, Ain(2) = 0, Ain(3) = 1, Ain(4) = 0

## Signals – Example (2)

---

- SIGNAL Byte: BIT\_VECTOR (7 downto 0);
- Note:
  - The signal "Byte" comprises eight bit objects.
  - The assignment statement:  
    Byte <= "10011000";  
Result in Byte(7)=1, Byte(6)=0, Byte(5)=0,  
Byte(4)=1, Byte(3)=1, Byte(2)=0, Byte(1)=0,  
Byte(0)=0

## Signals

---

- STD\_LOGIC & STD\_LOGIC\_VECTOR types
  - STD\_LOGIC type provides more flexibility than the BIT type.
  - To use this type, we must include these statements in VHDL files.
    - LIBRARY IEEE;
    - USE IEEE.STD\_LOGIC\_1164.ALL;
  - Note: These statements provide the access to the std\_logic\_1164 package, which defines the STD\_LOGIC type.

## IEEE Standard Logic Type

---

```
type STD_ULOGIC is (  
    'U' , -- uninitialized  
    'X' , -- strong 0 or 1 (= unknown)  
    '0' , -- strong 0  
    '1' , -- strong 1  
    'Z' , -- high impedance  
    'W' , -- weak 0 or 1 (= unknown)  
    'L' , -- weak 0  
    'H' , -- weak 1  
    '-' , -- don't care);
```

- 9 different signal states
- The new type is implemented as enumerated type by extending the existing '0' and '1' symbols with additional ASCII characters.
- Superior simulation results
- Bus modelling
- The 'u' symbol is the leftmost symbol of the declaration, i.e. it will be used as initial value during simulation.

- Defined in package 'IEEE.std\_logic\_1164'
- Similar data type 'std\_logic' with the same values
- Array types available: 'std\_(u)logic\_vector', similar to 'bit\_vector'

## Variables

---

- A **variable**, unlike a SIGNAL, does not necessarily represent a wire in a circuit.
- Variables can be **used in sequential areas only**
  - The scope of a variable is the process or the subprogram.
  - A variable in a subprogram does not retain its value between calls.
- **Variable assignment is immediate, not scheduled.**

## Logic Operators

---

- **and, or, xor, xnor, nand, nor, not**
- Example:
  - `Z <= A and B and C;`
  - `Z <= (not A and B) or (A and not B);`

## Concurrency

---

- VHDL concurrent statements execute in a **concurrent** fashion, i.e., statements execute only when associated signals change value.
- There is no master, procedural flow of control; each concurrent statement execute in a *nonprocedural stimulus/response*.

```
ENTITY example1 IS
    PORT (x1, x2, x3 : IN    BIT;
          f : OUT    BIT);
END example1;

ARCHITECTURE logicFunc OF example1 IS
    SIGNAL a1, b2: BIT;
    BEGIN
        -- Concurrent signal assignment statements
        a1 <= x1 AND x2;
        b1 <= NOT x2 AND x3;
        f <= a1 NOR b1;
    END logicFunc;
```

## VHDL Model

---

- **Structural model:** describe how it is composed of subsystems
  - Component declaration and instantiation
- Behavioral model: describe the function of entity in an abstract way


## Structural Modeling

---

- The **STRUCTURE** architecture describes the schematic for the majority logic by defining the *interconnection of components*
- Components are associated with design entities describing the **AND** and **OR** switching algebra operations.
- Use **component statement** in structural statement description.



## Hierarchical Model Layout

 

Full adder: 2 halfadders + 1 OR-gate

- A **module** can be assembled out of several submodules.
- A purely **structural architecture** does not describe any functionality and contains just a list of components, their instantiation and their interconnections.

## Component Declaration


```
entity FULLADDER is
  port (A,B, CARRY_IN: in bit;
        SUM, CARRY: out bit);
end FULLADDER;
```

```
architecture STRUCT of FULLADDER is
  signal W_SUM, W_CARRY1, W_CARRY2 : bit;
```

```
  component HALFADDER
    port (A, B : in bit;
          SUM, CARRY : out bit);
  end component;
```

```
  component ORGATE
    port (A, B : in bit;
          RES : out bit);
  end component;
```

```
begin
  ...
```

 

Full adder: 2 halfadders + 1 OR-gate

- In a component declaration, all module types, which will be used in the architecture, are declared.
- This declaration has to occur before the **'begin'** keyword of the architecture statement.
- The port list elements of the component are called **local elements**, they are **not signals**

## Component Declaration Format

---

-- The following is the FORMAT for declaring components.

**COMPONENT** component\_name

**PORT** ( clause ) ;

**END COMPONENT;**

The similarity between component declaration statement and entity declaration statement. *Both have a header, port clause and end statement.*

This similarity is not coincidental. Components are virtual design entities.

Component to entity association is provided by a configuration.

## Component Instantiation

architecture STRUCT of FULLADDER is

**component** HALFADDER

port (A, B : in bit;  
SUM, CARRY : out bit);

**end component;**

**component** ORGATE

port (A, B : in bit;  
RES : out bit);

**end component;**

**signal** W\_SUM, W\_CARRY1, W\_CARRY2: bit;

**begin** -- statement part

MODULE1: HALFADDER

**port map**( A, B, W\_SUM, W\_CARRY1 );

MODULE2: HALFADDER

**port map** ( W\_SUM, CARRY\_IN,  
SUM, W\_CARRY2);

MODULE3: ORGATE

**port map** ( W\_CARRY2, W\_CARRY1, CARRY );

**end STRUCT;**

- Component instantiations occur in the statement part of an architecture (after the keyword "begin").

- The choice of components is restricted to those that are already declared, either in the declarative part of the architecture or in a package.

- The connection of signals to the entity port:
  - Default: positional association, the first signal of the port map is connected to the first port from the component declaration.

## Component Instantiation: Named Signal Association

---

```
entity FULLADDER is
  port (A,B, CARRY_IN: in bit;
        SUM, CARRY: out bit);
end FULLADDER;
```

```
architecture STRUCT of FULLADDER is
```

```
  component HALFADDER
    port (A, B : in bit;
          SUM, CARRY : out bit);
  end component;
  ...
  signal W_SUM, W_CARRY1, W_CARRY2 : bit;
```

```
begin
```

```
  MODULE1: HALFADDER
    port map ( A => A,
              SUM => W_SUM,
              B => B,
              CARRY => W_CARRY1 );
end STRUCT;
```

- Named association:
  - left side: "formals"  
(port names from component declaration)
  - right side: "actuals"  
(architecture signals)
  - Independent of order in component declaration

## Syntax of the Component Instantiation Statement

---

**Label: component\_name**  
**[GENERIC MAP (association\_list)]**  
**[PORT MAP (association\_list) ] ;**


The label and component name are the only required elements of the component instantiation statement.

**GENERIC MAP** is optional if there are no generics declared within the entity declaration of the instantiated component or there is no need to override the declared generic.

**PORT MAP** describes how each component instance is connected to the rest of the system.
 
## Example 1 :

Write a VHDL description for the circuit in below figure. Use component instantiation statement and an internal signal x.



```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;
```

```
-- Entity declaration begins
```

```
ENTITY example2_6 IS  
    PORT (a, b, c : IN  STD_LOGIC;  
          d       : OUT STD_LOGIC);  
END example2_6;
```


```
ARCHITECTURE arch2_6 OF example2_6 IS
```

```
    COMPONENT and1  
        PORT ( p, q: IN  STD_LOGIC;  
              r   : OUT STD_LOGIC);  
    END COMPONENT;
```

```
    COMPONENT or1  
        PORT ( p, q: IN  STD_LOGIC;  
              r   : OUT STD_LOGIC);  
    END COMPONENT;
```

```
-- Declare signals to interconnect logic  
operators  
    SIGNAL x : BIT;
```
 
```
BEGIN  
    U1A : and1 PORT MAP ( a, b, x);  
    U2A : or1  PORT MAP ( x, c, d);  
END arch2_6;
```



```
Entity and1 IS
```

```
    PORT ( p, q : IN  STD_LOGIC;  
          r   : OUT STD_LOGIC);
```

```
END and1;
```

```
ARCHITECTURE arch OF and1 IS  
BEGIN
```

```
    r <= p AND q;  
END arch;
```

---

```
LIBRARY IEEE;  
USE IEEE.STD_LOGIC_1164.ALL;  
-- Entity declaration begins  
ENTITY example2_6 IS  
    PORT (a, b, c : IN STD_LOGIC;  
          d   : OUT STD_LOGIC);  
END example2_6;  
-- entity declaration ends. The PORT clause  
declares signals (a, b, c, d) that interfaces the  
module to the outside world.
```

---

#### **ARCHITECTURE arch2\_6 OF example2\_6 IS**

```
-- component declaration portion of architecture.  
-- Before a component is instantiated in a logic circuit, it must first be declared.  
-- The two components to be declared are an AND and OR gate given the names  
"and1" and "or1" respectively.
```

```
COMPONENT and1  
    PORT ( p, q : IN   STD_LOGIC;  
          r   : OUT STD_LOGIC);  
END COMPONENT;
```

```
COMPONENT or1  
    PORT ( p, q : IN   STD_LOGIC;  
          r   : OUT STD_LOGIC);  
END COMPONENT;
```

- **signal declaration portion** of architecture.
- ~~Declare signals to interconnect logic operators~~
- The circuit has an internal signal with the name x which is used by both components, this signal should also be declared prior to its usage in the architecture body.

**SIGNAL x : BIT;**

- **Component Instantiation portion** of architecture
- The component instantiation statement connect logic operators to describe schematic.

**BEGIN**


**U1A : and1 PORT MAP ( a, b, x );**

**U2A : or1 PORT MAP ( x, c, d );**

**END arch2\_6;**
 
## Example 2:

Write a VHDL code for the circuit shown below. The inputs to the circuit is x1, x2, x3, and the output is f ?




## Example 2: VHDL code- Behavior

```

entity example1 is
    port (x1, x2, x3: in bit;
          f: out bit);
end example1;

 architecture behavior of example1 is
    begin -- Architecture statement region
        f <= (x1 and x2) nor (not x2 and x3);
    end behavior;
  
```



• **behavior**: user-defined name

## Example 2: VHDL code-Structure

```

entity example1 is
    port (x1, x2, x3: in bit;
          f: out bit);
end example1;


architecture structure of example1 is
    component and is
        port (a, b: in bit; f: out bit);
    end component and;

    component nor is
        port (a,b: in bit; f: out bit);
    end component nor;


    component inv is
        port (a: in bit; f: out bit);
    end component inv;

    signal x2bar,u1aout,u5aout: bit;

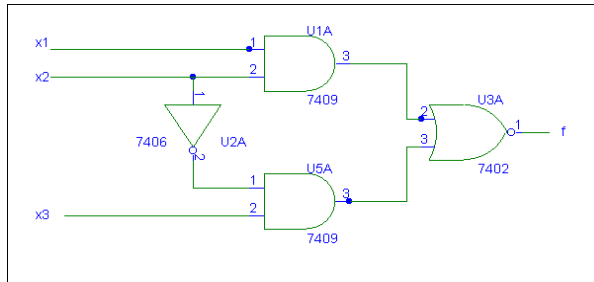    begin
        u1a: component and port map(x1,x2,u1aout)
        u2a: component inv port map(x2,x2bar);
        u3a: component nor port map(u1aout,u5aout,f);
        u5a: component and port map (x2bar,x3,u5aout);
    end structure;
  
```



## Example 3: Multiply-Accumulator

 

A two-input multiply accumulator device: multiply two 16-byte data. Internal signals are: `reg_in1`, `reg_in2`, `mul`, `reg_mul`, `adder`, `accum`. Two serial-to-parallel registers `u1` and `u2` convert the input bit stream of the data into a 16-wide data. The multiplier `u3` sends its output to the adder `u5` via register `u4`.

These components are found in the package `ECE_252_PACKAGE` which is found in the library `WORK`.

The `USE` statement makes all the components in this package visible to our design. ■

```
LIBRARY WORK;
```

```
USE WORK.ECE_252_PACKAGE.ALL;
```

```
ENTITY mac IS
```

```
  GENERIC (tco : time := 10 ns);
```

```
  PORT (in1, in2 : IN BIT_VECTOR (15 DOWNTO 0);
```

```
        clk      : IN BIT;
```

```
        output   : OUT BIT_VECTOR(31 DOWNTO 0);
```

```
END mac;
```



### ARCHITECTURE structure OF mac IS

-- component declaration part, components include a register called **reg**,  
-- an adder called **adder**, a multiplier called **multiply**, a buffer called **buf**

```
COMPONENT reg
  GENERIC ( width : integer := 16);
  PORT ( d : IN BIT_VECTOR (width-1 DOWNT0 0);
        clk : IN BIT;
        q : OUT BIT_VECTOR (width-1 DOWNT0 0));
END COMPONENT;

COMPONENT adder
  PORT (port1, port2 : IN BIT_VECTOR (31 DOWNT0 0);
        output : OUT BIT_VECTOR (31 DOWNT0 0));
END COMPONENT;

COMPONENT multiply
  PORT (port1, port2 : IN BIT_VECTOR (15 DOWNT0 0);
        output : OUT BIT_VECTOR (31 DOWNT0 0));
END COMPONENT;

COMPONENT buf
  PORT ( input : IN BIT_VECTOR (31 DOWNT0 0);
        output : OUT BIT_VECTOR (31 DOWNT0 0));
END COMPONENT;
```

-- signal declaration portion of architecture

```
SIGNAL reg_in1, reg_in2 : BIT_VECTOR (15 DOWNT0 0);
SIGNAL mul, reg_mul, adder, accum : BIT_VECTOR (31
DOWNT0 0);
```

-- Component instantiation and logic interconnection

```
BEGIN
u1: reg GENERIC MAP(16) PORT MAP ( in1, clk, reg_in1);
u2: reg GENERIC MAP(16) PORT MAP ( in2, clk, reg_in2);
u3: multiply PORT MAP (reg_in1, reg_in2, mul);
u4: reg GENERIC MAP(32) PORT MAP (mul, clk, reg_mul);
u5: adder PORT MAP (reg_mul, accum, adder);
u6: reg GENERIC MAP(32) PORT MAP (adder, clk, accum);
u7: buf PORT MAP (accum, output)
END structure;
```