

ECE 3401 Lecture 11


Sequential Circuits

Overview of Sequential Circuits


- **Storage Elements**
 - Sequential circuits
 - Storage elements: Latches & Flip-flops
 - Registers and counters
- Circuit and System Timing
- Sequential circuit description and analysis:
State tables & State diagrams

Sequential Circuits

 
- A Sequential circuit contains:
 - Storage elements: Latches or Flip-Flops
 - Combinational Logic: implements a multiple-output switching function
 - *Next state function:* $\text{Next State} = f(\text{Inputs, State})$
 - *Output function: two types*
 - Mealy : $\text{Outputs} = g(\text{Inputs, State})$
 - Moore: $\text{Outputs} = h(\text{State})$




Latches

 


Basic S-R latch

 

Basic \bar{S} - \bar{R} latch

 



Clocked S-R latch

 

D latch


Edge-Triggered D Flip-Flop

  - The edge-triggered D flip-flop is the master-slave D flip-flop
- The change of Q is associated with the negative edge at the end of the pulse - *negative-edge triggered flip-flop*



Flip-flop Behavior Example

 - Use the characteristic tables to find the output waveforms for the flip-flops shown:



Modeling of Flip-Flops

```
Library IEEE;  
use IEEE.Std_Logic_1164.all;
```

```
entity FLOP is  
  port (D, CLK : in std_logic;  
        Q : out std_logic);  
end FLOP;
```

```
architecture A of FLOP is  
begin  
  process  
  begin  
    wait until CLK'event and CLK='0';  
    Q <= D;  
  end process;  
end A;
```

- D Flip-flop controlled by a clock pulse edge.


Or:

```
process (clk)  
begin  
  if (clk='0') then  
    Q <= D;  
  end if;  
end process;
```

Direct Inputs

- At power up or at reset, sequential circuit usually is initialized to a known state before it begins operation
 - Done outside of the clocked behavior of the circuit, i.e., asynchronously.
 - Direct R/S inputs

 - For the example flip-flop shown
 - 0 applied to \bar{R} resets the flip-flop to the 0 state
 - 0 applied to \bar{S} sets the flip-flop to the 1 state



Positive Edge-Triggered D Flip-flop with Asynchronous Set/Reset

```
library IEEE;
use IEEE.std_logic_1164.all;

entity ASYNC_FF is
  port (D, CLK, SETN, RSTN : in std_logic;
        Q : out std_logic);
end ASYNC_FF;

architecture RTL of ASYNC_FF is
begin
  process (CLK, RSTN, SETN)
  begin
    if (RSTN = '1') then
      Q <= '0';
    elsif SETN = '1' then
      Q <= '1';
    elsif (CLK'event and CLK = '1') then
      Q <= D;
    end if;
  end process;
end RTL;
```

- It has a sensitivity list
- **If / elsif** – structure
 - The last **elsif** has an edge
 - No unconditional **else** branch

Registers

- Register: the simplest storage component in a computer, a bit-wise extension of a flip-flop.
- Registers can be classified into
 - Simple Registers
 - Parallel-Load Registers
 - Shift Registers

Simple Registers

Fig.1 A 4-bit Register: top – schematic, bottom – graphical symbol.


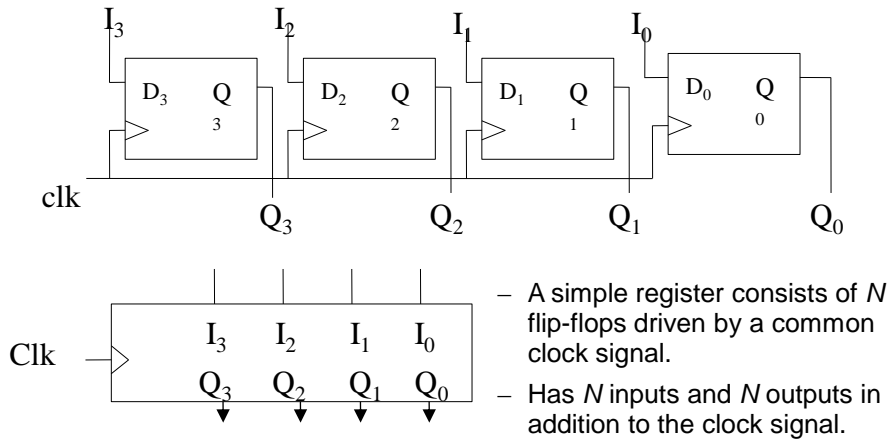


Fig.2 A 4-bit register with asynchronous preset and clear

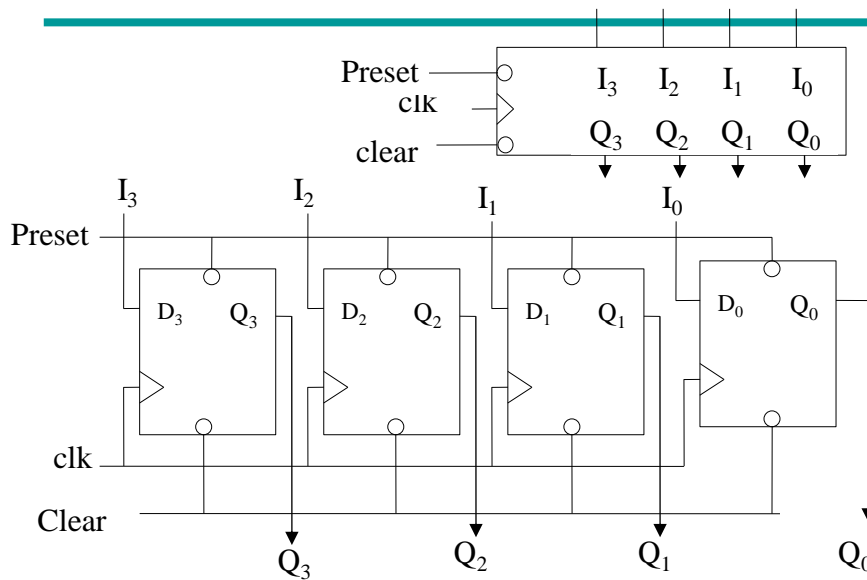

```

Library ieee;
USE ieee.std_logic_1164.all;
ENTITY simple_register IS
  GENERIC ( N : INTEGER := 4);
  PORT ( I : IN STD_LOGIC_VECTOR (N-1 DOWNTO 0);
        Clock, Clear, Preset : IN STD_LOGIC;
        Q : OUT STD_LOGIC_VECTOR (N-1 DOWNTO 0));
END simple_register;

ARCHITECTURE simple_memory OF simple_register IS
BEGIN
PROCESS (Preset, Clear, Clock)
BEGIN
  IF Preset = '0' THEN
    Q <= (OTHERS => '1');;
  ELSIF Clear = '0' THEN
    Q <= (OTHERS => '0');
  ELSIF (Clock'EVENT AND Clock = '1') THEN
    Q <= I;
  END IF;
END PROCESS;
END simple_memory;

```

Parallel Load Registers

- In the previous registers, new data is stored automatically on every rising edge of the clock.
- In most digital systems, the data is stored for several clock cycles before it is rewritten. For this reason it is useful to be able to control **WHEN** the data will be entered into a register.
 - Use a control signal called *Load* or *Enable*. This allows loading into a register known as a **parallel-load register**.

VHDL Code for Parallel-load Register

```

Library ieee;
USE ieee.std_logic_1164.all;
ENTITY load_enable IS
    GENERIC ( N : INTEGER := 4);
    PORT ( D : IN STD_LOGIC_VECTOR (N-1 DOWNT0 0);
          Clock, Resetrn, load : IN STD_LOGIC;
          Q : BUFFER STD_LOGIC_VECTOR(N-1 DOWNT0 0));
END load_enable;


```

```


ARCHITECTURE rtl OF load_enable IS
    SIGNAL state : std_logic_vector(N-1 DOWNT0 0);
BEGIN
    PROCESS (Resetrn, Clock) IS
        BEGIN
            IF Resetrn = '0' THEN
                state <= (OTHERS => '0');
            ELSIF (Clock'EVENT AND Clock = '1') THEN
                IF load = '1' THEN
                    state <= D;
                ELSE
                    state <= state;
                END IF;
            END IF;
        END PROCESS;
        Q <= state;
    END rtl;

```

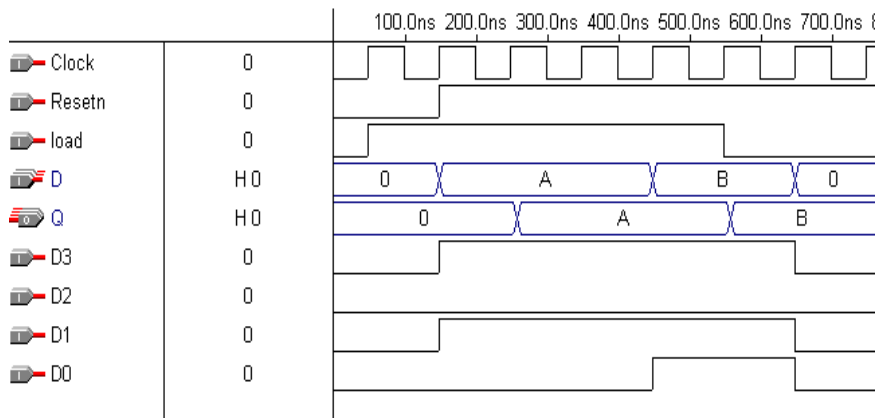Timing diagram for parallel-load register




Serial-in/Parallel-out Shift Register

 

(a) Graphic symbol


PRESENT STATE	NEXT STATE			
Shift	Q_3	Q_2	Q_1	Q_0
0	No change			
1	I_L	Q_3	Q_2	Q_1

(b) Operation table

 

(c) Register schematic


Parallel Load Shift Register

 

(a) Graphic symbol

PRESENT STATE		OPERATION	NEXT STATE			
S_1	S_0		Q_3	Q_2	Q_1	Q_0
0	0	No change	Q_3	Q_2	Q_1	Q_0
0	1	Load input	I_3	I_2	I_1	I_0
1	0	Shift left	Q_2	Q_1	Q_0	I_R
1	1	Shift right	I_L	Q_3	Q_2	Q_1

(b) Operation table

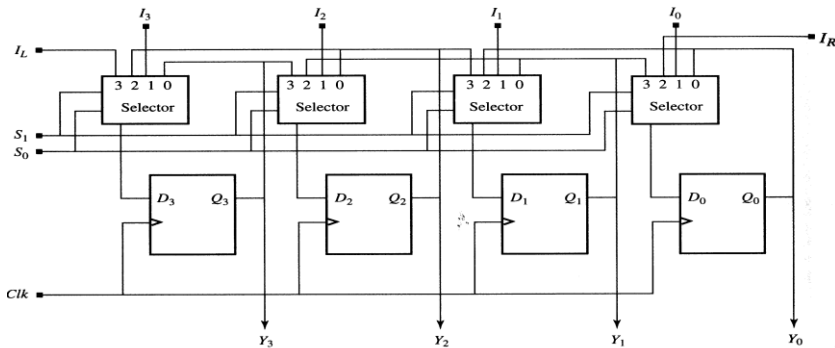

(c) Register schematic

Counters


- Counter: a special type of register that incorporates an incrementer or decremter, which allows it to count upward or downward.
- We shall examine VHDL code for the following counters:
 - Up counter
 - Down counter

VHDL for Up-Counter

```
Library ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
ENTITY upcount IS
    GENERIC ( N : INTEGER := 4 );
    PORT ( Clock, Resetn, Enable : IN STD_LOGIC;
          Q: BUFFER STD_LOGIC_VECTOR (N-1 DOWNT0 0));
END upcount;


ARCHITECTURE cnt OF upcount IS
    SIGNAL count : STD_LOGIC_VECTOR (N-1 DOWNT0 0);
BEGIN
    PROCESS (Resetn, Clock)
    BEGIN
        IF Resetn = '0' THEN
            count <= ( OTHERS => '0' );
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF Enable = '1' THEN
                count <= count +1;
            ELSE
                count <= count;
            END IF;
        END IF;
    END PROCESS;
    Q <= count;
END cnt;
```

Timing Diagram for Up-Counter

 


Synchronous Counters

 - Internal Logic
 - Incrementer: $Q+0$ or $Q+1$
- Contraction of a ripple carry adder with one operand fixed at 000X
- Symbol for Synchronous Counter




Symbol

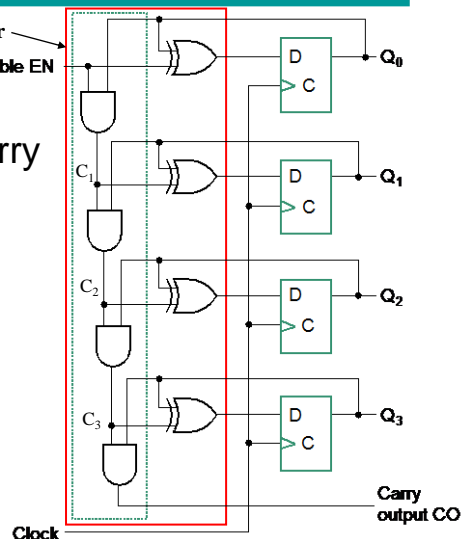

 (a) Logic Diagram-Serial Gating

Synchronous Counters (Contd.)

- Contraction of carry-lookahead adder
 - Reduce path delays
 - Called *parallel gating*
 - Lookahead can be used on COs and ENs to prevent long paths in large counters





Logic Diagram-Parallel Gating

Counter with Parallel Load

Load	Count	Action
0	0	Hold Stored Value
0	1	Count Up Stored Value
1	X	Load D

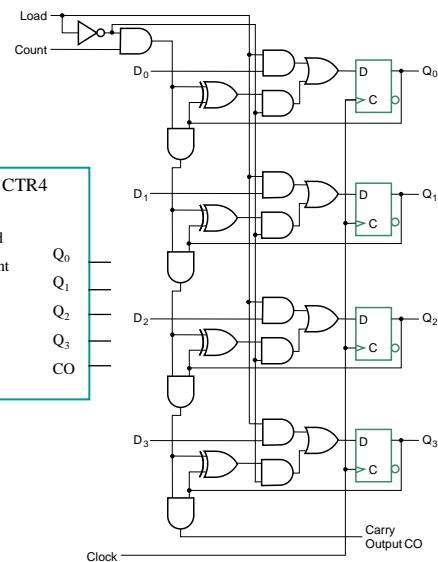 - Add path for input data D
 - enabled for Load = 1
- Add logic to:
 - When Load = 1 disable count logic (feedback from outputs)
 - When Load = 0 and Count = 1 enable count logic



BCD Counter

```
architecture Behavioral of bcd_counter is
    signal regcnt : std_logic_vector(3 downto 0);
begin
    count: process(reset,clk) is
        begin
            if ( reset='1' ) then
                regcnt <= "0000";
            elsif ( clk'event and clk='1' ) then
                regcnt <= regcnt+1;
                if (regcnt = "1001") then
                    regcnt <= "0000";
                end if;
            end if;
        end process;
    end Behavioral;
```

