

ECE 3401 Lecture 12

Sequential Circuits (II)

Overview of Sequential Circuits

- Storage Elements
 - Sequential circuits
 - Storage elements: Latches & Flip-flops
 - **Registers and counters**

- Circuit and System Timing

- Sequential circuit analysis and description:
State tables & State diagrams

Counters


- Counter: a special type of register that incorporates an incremter or decremter, which allows it to count upward or downward.
- We shall examine VHDL code for the following counters:
 - Up counter
 - Down counter

VHDL for Up-Counter

```
Library ieee;
USE ieee.std_logic_1164.all;
USE ieee.std_logic_unsigned.all;
ENTITY upcount IS
    GENERIC ( N : INTEGER := 4 );
    PORT ( Clock, Resetn, Enable : IN STD_LOGIC;
          Q: BUFFER STD_LOGIC_VECTOR (N-1 DOWNTO 0));
END upcount;


ARCHITECTURE cnt OF upcount IS
    SIGNAL count : STD_LOGIC_VECTOR (N-1 DOWNTO 0);
BEGIN
    PROCESS (Resetn, Clock)
    BEGIN
        IF Resetn = '0' THEN
            count <= ( OTHERS => '0' );
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF Enable = '1' THEN
                count <= count +1;
            ELSE
                count <= count;
            END IF;
        END IF;
    END PROCESS;
    Q <= count;
END cnt;
```

Timing Diagram for Up-Counter

 


Synchronous Counters

 - Internal Logic
 - Incrementer: $Q+0$ or $Q+1$
- Contraction of a ripple carry adder with one operand fixed at 000X
- Symbol for Synchronous Counter




Symbol

 

 (a) Logic Diagram-Serial Gating

Synchronous Counters (Contd.)


- Contraction of carry-lookahead adder
 - Reduce path delays
 - Called *parallel gating*
 - Lookahead can be used on COs and ENs to prevent long paths in large counters



Counter with Parallel Load


Load	Count	Action
0	0	Hold Stored Value
0	1	Count Up Stored Value
1	X	Load D

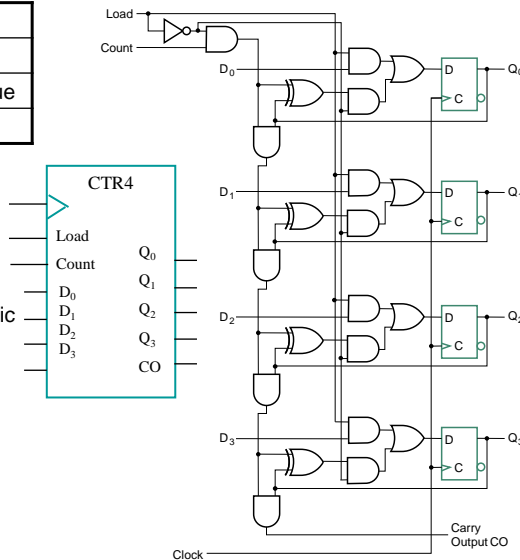- Add path for input data D
 - enabled for Load = 1
- Add logic to:
 - When Load = 1 disable count logic (feedback from outputs)
 - When Load = 0 and Count = 1 enable count logic



BCD Counter

```
architecture Behavioral of bcd_counter is
    signal regcnt : std_logic_vector(3 downto 0);
begin
    count: process(reset,clk) is
        begin
            if (reset='1') then
                regcnt <= "0000";
            elsif ( clk'event and clk='1') then
                regcnt <= regcnt+1;
                if (regcnt = "1001") then
                    regcnt <= "0000";
                end if;
            end if;
        end process;
    end Behavioral;
```

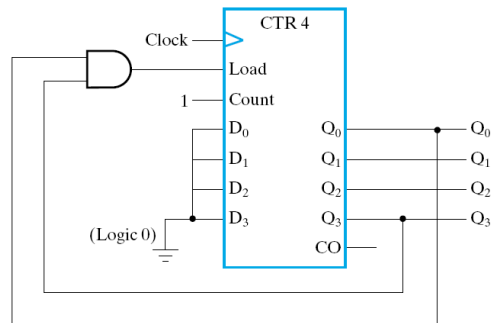


Overview of Sequential Circuits


- **Storage Elements**
 - Sequential circuits
 - Storage elements: Latches & Flip-flops
 - Registers and counters
- **Circuit and System Timing**
- Sequential circuit analysis and description:
State tables & State diagrams

Flip-Flop Timing Parameters

 - t_w - clock pulse width
- t_s - setup time: Equal to a time interval that is generally much less than the width of the triggering pulse
- t_h - hold time - Often equal to zero
- t_{px} - propagation delay
 - Same parameters as for gates except
 - Measured from clock edge that triggers the output change to the stabilization of the output to a new value





Edge-triggered (negative edge)

 

Triggered D


Circuit and System Level Timing

  - Consider a system comprised of ranks of flip-flops connected by logic
- If the clock period is too short, some data changes will not propagate through the circuit to next flip-flop inputs before the setup time interval begins



Circuit and System Level Timing (Contd.)

 - Timing components along a path from flip-flop to flip-flop



- Timing Equations

$$t_p = t_{slack} + (t_{pd,FF} + t_{pd,COMB} + t_s)$$

$$t_p \geq \max (t_{pd,FF} + t_{pd,COMB} + t_s)$$

for all paths from flip-flop output to flip-flop input

Calculation of Allowable $t_{pd,COMB}$


- Compute the allowable $t_{pd,COMB}$ for a circuit using edge-triggered flip-flops
- Parameters
 - $t_{pd,FF}(\max) = 1.0$ ns
 - Clock frequency = 250 MHz, $t_p = 1/\text{clock frequency} = 4.0$ ns
 - $t_s(\max) = 0.3$ ns for edge-triggered flip-flops
 - for a gate, average $t_{pd} = 0.3$ ns
- Calculations:
 - Edge-triggered: $4.0 \geq 1.0 + t_{pd,COMB} + 0.3$
 - $\Rightarrow t_{pd,COMB} \leq 2.7$ ns, approximately 9 gates allowed on a path

Overview of Sequential Circuits

- Storage Elements
 - Sequential circuits
 - Storage elements: Latches & Flip-flops
 - Registers and counters
- Circuit and System Timing
- Sequential circuit analysis and description:
State tables & State diagrams

 
Example 1

- Input: $x(t)$
- Output: $y(t)$
- State: $(A(t), B(t))$
- Output Function?
 - $y(t) = \overline{x(t)}(B(t) + A(t))$
- Next State Function?
 - $A(t+1) = A(t)x(t) + B(t)x(t)$
 - $B(t+1) = \overline{A(t)}x(t)$



 Example 1 (Contd.)

- Where in time are inputs, outputs and states defined?



$$y(t) = \overline{x(t)}(B(t) + A(t))$$

$$A(t+1) = A(t)x(t) + B(t)x(t)$$

$$B(t+1) = \overline{A(t)}x(t)$$


State Table Characteristics

- The state table can be filled in using the next state and output equations: $A(t+1) = A(t)x(t) + B(t)x(t)$, $B(t+1) = \overline{A(t)}x(t)$
 $y(t) = \overline{x(t)}(B(t) + A(t))$

Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	y(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

State Diagram

Present State		Input	Next State		Output
A(t)	B(t)	x(t)	A(t+1)	B(t+1)	v(t)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

 

Design Procedure for Sequential Circuits

- **Formulation:** Obtain a state diagram or state table
- **State Assignment:** Assign binary codes to the states
- **Flip-Flop Input Equation Determination:** Select flip-flop types, derive flip-flop input equations from next state entries in the table
- **Output Equation Determination:** Derive output equations from output entries in the table
- **Optimization** - Optimize the equations
- **Technology Mapping** - Find circuit from equations and map to flip-flops and gate technology
- **Verification** - Verify correctness of final design

Formulation: Finding a State Diagram


- State: an abstraction of the history of past-applied inputs to the circuit (including power-up or system reset)
 - Asynchronous reset normally resets to the initial state
- In specifying a circuit, states remember meaningful properties of past input sequences that are essential to predicting future output values, e.g.:
 - State A represents the fact that a 1 input has occurred among the past inputs.
 - State B represents the fact that a 0 followed by a 1 have occurred as the most recent past two inputs.

Example: Sequence Recognizer Procedure


- A sequence recognizer: produces an output value '1' whenever a prescribed pattern of inputs occur in sequence
- Steps:
 - Begin in an initial state (typically "reset" state), when NONE of the initial portion of the sequence has occurred
 - Add states
 - that recognize each successive symbol occurring
 - the final state represents the input sequence occurrence.
 - Add state transition arcs which specify what happens when a symbol *not* in the proper sequence has occurred.
 - Add other arcs on non-sequence inputs which transition to states.
 - The last step is required because the circuit must recognize the input sequence *regardless of where it occurs within the overall sequence applied since "reset."*

 Example: Recognize 1101

- Define states for the sequence to be recognized
- Starting in the initial state ("A"):




 - Finally, output 1 on the arc from D means the sequence has been recognized,
 - To what state should the arc from state D go? Remember: 1101101 ?
 - The final 1 in the recognized sequence 1101 is a sub-sequence of 1101. It follows a 0 which is not a sub-sequence of 1101. Thus it should represent *the same state reached from the initial state after a first 1 is observed*.



 Example: Recognize 1101 (Contd.)



- The other arcs are added to each state for inputs not yet listed. Which arcs are missing?
 - State transition arcs must represent the fact that an input subsequence has occurred.
 - Note that the 1 arc from state C back to C implies that State C means *two or more 1's have occurred*.




Present State	Next State		Output	
	x=0	x=1	x=0	x=1
A	A	B	0	0
B	A	C	0	0
C	D	C	0	0
D	A	B	0	1

  Example: Moore Model

- For Moore Model, outputs are associated with states. Arcs now show only state transitions
- Add a new state E to produce the output 1
 - State E produces the same behavior in the future as state B, but it gives a different output at the present time. Thus these states do represent a *different abstraction* of the input history.
- The Moore model for a sequence recognizer usually has *more states* than the Mealy model.



Example: Moore Model (Contd.)

 

Present State	Next State		Output y
	x=0	x=1	
A	A	B	0
B	A	C	0
C	D	C	0
D	A	E	0
E	A	C	1

VHDL Example: Sequential Recognizer

- VHDL for the sequential recognizer follows


```
library ieee;
use ieee.std_logic_1164.all;
entity seq_rec is
port (CLK, RESET, X: in std_logic;
      Z: out std_logic);
end seq_rec;

architecture process_3 of seq_rec is
type state_type is (A, B, C, D);
signal state, next_state: state_type;
begin
```

VHDL Example (Contd.)

--process 1: implements positive edge-triggered flipflop with asynchronous reset
 
```
state_register: process (CLK, RESET)
begin
if(RESET = '1') then
state <= A;
elsif (CLK'event and CLK = '1') then
state <= next_state;
end if;
end process;
```



--process 2: implement output as function of input X and state

```
output_function: process (X, state)
begin
case state is
when A => Z <= '0';
when B => Z <= '0';
when C => Z <= '0';
when D => if X = '1' then Z <= '1';
else Z <= '0'; end if;
end case;
end process;
```

VHDL Example: (Process 3)

--process 3: next state-function implemented as a function of input X and state
next_state_function: process (X, state)

```
begin
case state is
when A =>
if X = '1' then next_state <= B;
else next_state <= A;
end if;
when B =>
if X = '1' then next_state <= C;
else next_state <= A;
end if;
when C =>
if X = '1' then next_state <= C;
else next_state <= D;
end if;
when D =>
if X = '1' then next_state <= B;
else next_state <= A;
end if;
end case;
end process;

end architecture;
```

