

ECE 3401 Lecture 14


Datapath & Control Unit (II)

Overview

- Datapath and control
- Microoperations
 - Register transfer operations
 - Microoperations - arithmetic, logic, and shift
 - Register cell design
 - Multiplexer-based single register transfers
 - Sequential Circuit Design
 - Serial transfers and microoperations
- Sequencing and control

Multiplexer-Based Single Register Transfers

 - MUX connected to register outputs produce flexible transfer structures
- Transfers: $K_1: R_0 \leftarrow R_1$
 $K_2 K_1: R_0 \leftarrow R_2$




Register Design

- Assume: a register consists of identical cells
- Register design can be approached as follows:
 - Design a representative cell for the register
 - Make copies of the cell and connect together to form the register
 - Applying appropriate “boundary conditions” to cells that need to be different and contract if appropriate
- Register cell design is the first step of the above process


Approach I: Multiplexer-based

- An n-input multiplexer with a variety of sources and functions
- Load enable by OR of control signals K_0, K_1, \dots, K_{n-1} (for 00...0, no load)
- Use encoder + multiplexer to select sources and/or transfer functions

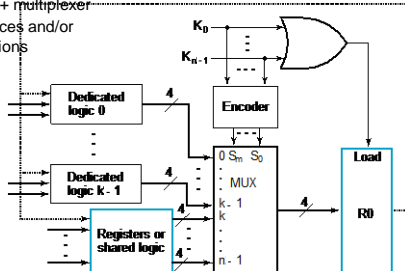

Example 1: Register Cell Design

- Register A (m-bits) Specification:
 - Data input: B; Control inputs (CX, CY): (0,0), (0,1), (1,0)
 - Register transfers:
 - $CX: A \leftarrow B \vee A$; $CY: A \leftarrow B \oplus A$; Hold state: (0,0)
- Load Control: $Load = CX + CY$
- Since all control combinations appear as if encoded (0,0), (0,1), (1,0), can use multiplexer without encoder:
 - $S_1 = CX$
 - $S_0 = CY$
 - $I_0 = A_i$
 - $I_1 = A_i \leftarrow B_i \oplus A_i$
 - $I_2 = A_i \leftarrow B_i \vee A_i$
 - Hold A
 - $CY = 1$
 - $CX = 1$

 

Approach II: Sequential Circuit Design

- Find a state diagram or state table
- For optimization:
 - Use K-maps for up to 4 to 6 variables
 - Otherwise, use computer-aided or manual optimization

Example 1 Again


- State Table for D_i :

	Hold	$A_i \vee B_i$		$A_i \oplus B_i$	
A_i	CX = 0 CY = 0	CX = 1 CY = 0 $B_i = 0$	CX = 1 CY = 0 $B_i = 1$	CX = 0 CY = 1 $B_i = 0$	CX = 0 CY = 1 $B_i = 1$
0	0	0	1	0	1
1	1	1	1	1	0

- Four variables (CX, CY, A, B) should give a total of 16 state table entries
- By using:
 - Combinations of variable names and values
 - Don't care conditions (for CX = CY = 1)
 only 12 entries are required to represent the 16 entries

 Example 1 Again (Contd.)

- K-map - Use variable ordering CX, CY, A_i , B_i and assume a D flip-flop



Example 1 Again (Contd.)

- The resulting SOP equation:


$$D_i = CX B_i + CY \bar{A}_i B_i + A_i \bar{B}_i + \bar{C}Y A_i$$

$$= CX B_i + \bar{A}_i (CY B_i) + A_i (CY \bar{B}_i)$$

$$= CX B_i + A_i \oplus (CY B_i)$$
 The gate input cost per cell = 13
- The gate input cost per cell for the previous version is:
 - Per cell: 19
 - Shared decoder logic: 8
- Cost gain by sequential design > 6 per cell
- Also, no Enable on the flip-flop makes it cost less

Serial Transfers and Microoperations

 - Serial Transfers
 - Used for "narrow" transfer paths
 - Example 1: Telephone or cable line
 - Parallel-to-Serial conversion at source
 - Serial-to-Parallel conversion at destination
- Serial microoperations
 - Example 1: Addition
 - A low cost way
 - Loss in performance



Overview

- Datapath and control
- Microoperations
- Sequencing and control
 - Algorithmic State Machines (ASM)
 - ASM chart
 - Timing considerations
 - ASM chart examples: Binary multiplier
 - Hardwired Control
 - Control design methods
 - Sequence register and decoder
 - One flip-flop per state
 - Microprogrammed control

Control Unit Types

- Two distinct classes:
 - Programmable
 - Non-programmable.
- A programmable control unit:
 - An external memory array for storing instructions and control information
 - A program counter (PC) register points to the next instruction to be executed
 - Decision logic for determining the sequence of operations and logic to interpret the instructions
- A non-programmable control unit: does not fetch instructions from a memory and is not responsible for sequencing instructions


Algorithmic State Machines

- The function of a sequential circuit can be represented by a state table or a state diagram.
- An Algorithmic State Machine (ASM) is a flowchart-like way to specify state diagrams for sequential logic and, optionally, actions performed in a datapath.
 - A flowchart is a way of showing actions and control flow in an algorithm.
 - An ASM explicitly specifies a sequence of actions and their timing relationships
 - An ASM chart directly leads to a hardware realization
- Primitives:
 - State Box (a rectangle)
 - Decision Box
 - Scalar (a diamond)
 - Vector (a hexagon)
 - Conditional Output Box (an oval)

State Box


- A rectangle with:
 - The symbolic name for the state
 - An optional state code
 - Containing register transfer operations, and outputs activated within or while leaving the state

 - The symbolic name for the state marked outside the upper left top
- An optional state code, if assigned, outside the upper right top




Decision Box

 - Scalar : A diamond with:
 - One input path (entry point).
 - One input condition that is tested.
 - A TRUE/FALSE exit path (logic 1/0).




 - Vector: A hexagon with:
 - One input path (entry point).
 - A vector of input conditions tested.
 - Up to 2^n output paths. The path taken has a binary vector value that matches the vector input condition



Conditional Output Box

 - An oval with:
 - One input path from a decision box(es)
 - One output path
 - Register transfers or outputs that occur only if the conditional path to the box is taken.
- Transfers and outputs
 - in a state box are Moore type - dependent only on state
 - in a conditional output box are Mealy type - dependent on both state and inputs




Connecting Boxes Together

- By connecting boxes together, we see the power of expression.


- What are the:

 - Inputs? start
- Outputs? Avail, Init
- Conditional Outputs?
- Transfers? $A < 0$, $PC < 0$
- Conditional Transfers? INIT, transfer: $PC < 0$




ASM Blocks

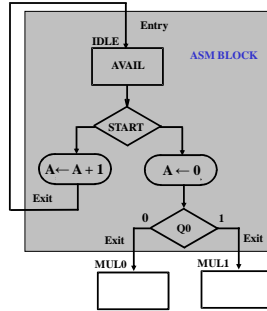- One state box along with all decision and conditional output boxes connected to it, called an **ASM Block**. i.e., the ASM Block includes all items on the path from the current state to the same or other states.




ASM Timing

 - Outputs appear while in the state
- Register transfers and conditional outputs occur at the clock while exiting the state - New value occur in the next state!



Multiply Overview

 - Binary multiplication is just a *bunch* of left shifts and adds



©2004 Morgan Kaufmann Publishers 21


Multiplier Example

- Example: (101×011) Base 2

- Partial products are: 101×0 , 101×1 , and 101×1

$$\begin{array}{r}
 101 \text{ multiplicand} \\
 \times 011 \text{ multiplier} \\
 \hline
 101 \\
 000 \\
 101 \\
 \hline
 001111
 \end{array}$$

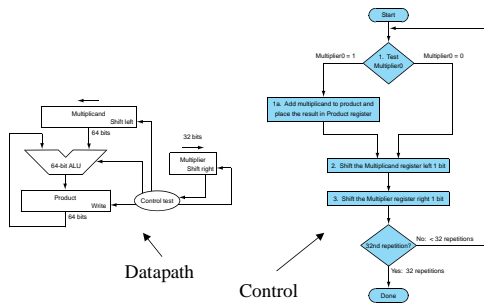
Multiplication: Implementation (version 1)



©2004 Morgan Kaufmann Publishers 23


Unsigned shift-add multiplier (version 1)

 - 64-bit Multiplicand reg, 64-bit ALU, 64-bit Product reg, 32-bit multiplier reg



Multiplier = datapath + control




©2004 Morgan Kaufmann Publishers 24

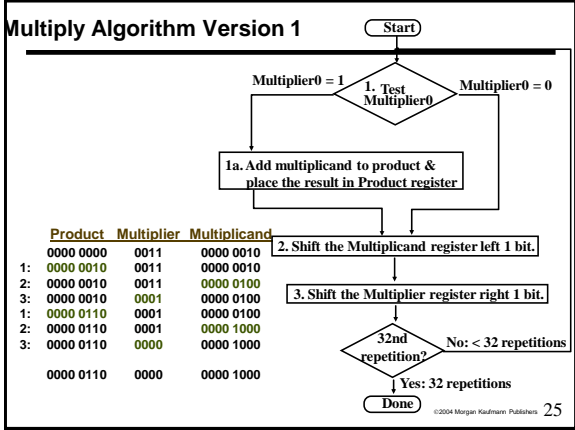

Observations on Multiply Version 1

- 1 clock per cycle => ≈ 100 clocks per multiply because of 32 repetitions, 3 steps in one repetition
 - Ratio of add/sub to multiply is from 5:1 to 100:1
 - Slow
- 0's inserted in the rightmost bit of multiplicand as shifting left
 - => least significant bits of product never changed once formed
- 1/2 bits in multiplicand always 0
 - MSB are 0s at the beginning
 - 0 is inserted in LSB as multiplicand shifting left
 - => 64-bit multiplicand register is wasted
 - => 64-bit adder is wasted
- **Instead of shifting multiplicand to left, let's shift product to right**

©2004 Morgan Kaufmann Publishers 26

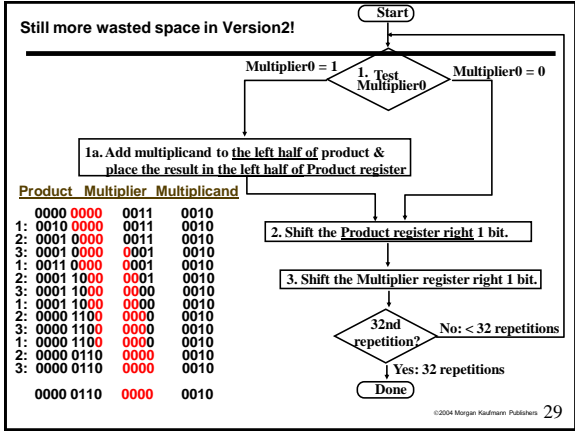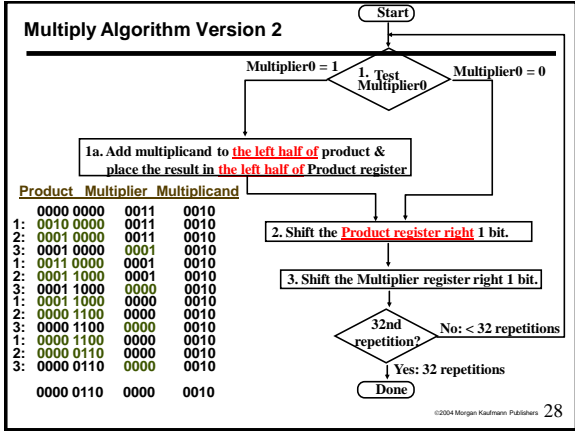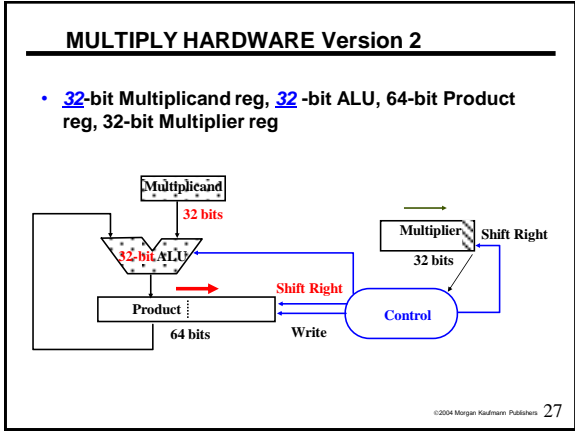


Observations on Multiply Version 2

- Product register wastes space that exactly matches size of multiplier
 - => **combine Multiplier register and Product register**

©2004 Morgan Kaufmann Publishers 30

MULTIPLY HARDWARE Version 3

 
- 32-bit Multiplicand reg, 32-bit ALU, 64-bit Product reg, (0-bit Multiplier reg)



©2004 Morgan Kaufmann Publishers 31


Version 3

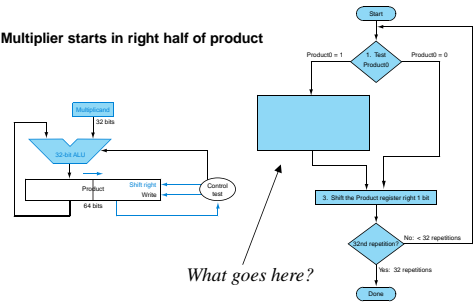- Multiplier starts in right half of product



©2004 Morgan Kaufmann Publishers 32


Multiply Algorithm Version 3

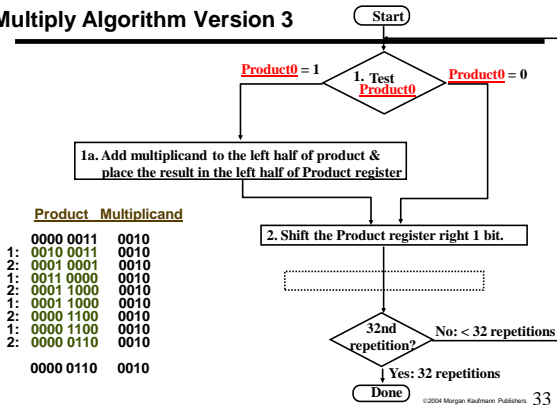

©2004 Morgan Kaufmann Publishers 33

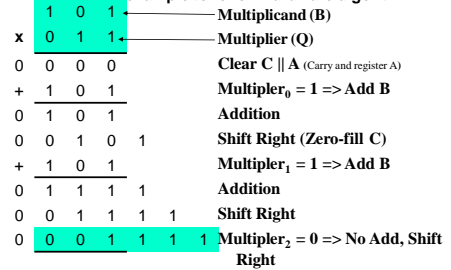
Example (1 0 1) x (0 1 1) Again

- Reorganizing example to follow hardware algorithm:



©2004 Morgan Kaufmann Publishers 34

Multiplier Example: Block Diagram

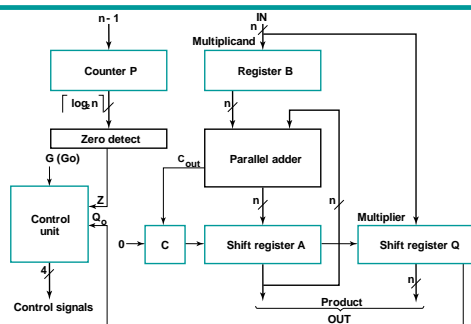

Multiplexer Example: Operation

- The multiplicand is loaded into register B.
- The multiplier is loaded into register Q.
- When G becomes 1, register C || A is initialized to 0.
- Down Counter P is initialized to n - 1 (n = number of bits in multiplier)
- The partial products are formed in register C || A || Q.
- Each multiplier (Q) bit, beginning with the LSB, is processed (if bit is 1, B is added to partial product of A; if bit is 0, do nothing)
- C || A || Q is shifted right using the shift register
 - Partial product bits fill vacant locations in Q as multiplier is shifted out
 - If overflow during addition, the outgoing carry is recovered from C during the right shift
- Steps 6 and 7 are repeated until P = 0 as detected by Zero detect.