

ECE 3401 Lecture 15


ASM-based Datapath/Control Design

Overview

- Datapath and control
- Microoperations
- Sequencing and control
 - Algorithmic State Machines (ASM)
 - ASM chart
 - Timing considerations
 - ASM chart examples: Binary multiplier
 - Hardwired Control
 - Control design methods
 - Sequence register and decoder
 - One flip-flop per state
 - Microprogrammed control

2

Multiplier Example: ASM Chart

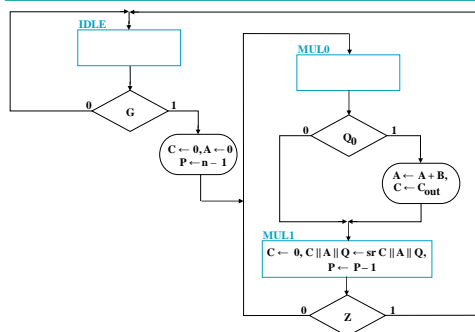

3

Multiplier Example: ASM Chart (Contd.)

- Three states employed here:
 - IDLE state:
 - input G is used as the condition for starting the multiplication
 - C, A, and P are initialized
 - MUL0 state: conditional addition is performed based on the value of Q_0 .
 - MUL1 state:
 - right shift is performed to capture the partial product and position the next bit of the multiplier in Q_0
 - Down counter $P = P - 1$
 - $P=0$ is used to sense completion or continuation of the multiplication.

4

Multiplier Example: Control Signal Table

Control Signals for Binary Multiplier

Block Diagram Module	Microoperation	Control Signal Name	Control Expression
Register A:	$A \leftarrow 0$	Initialize	IDLE · G
	$A \leftarrow A + B$	Load	MUL0 · Q_0
	$C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	Shift_dec	MUL1
Register B:	$B \leftarrow IN$	Load_B	LOADB
Flip-Flop C:	$C \leftarrow 0$	Clear_C	IDLE · G + MUL1
	$C \leftarrow C_{out}$	Load	—
Register Q:	$Q \leftarrow IN$	Load_Q	LOADQ
	$C \parallel A \parallel Q \leftarrow sr C \parallel A \parallel Q$	Shift_dec	—
Counter P:	$P \leftarrow n - 1$	Initialize	—
	$P \leftarrow P - 1$	Shift_dec	—

5


Multiplier Example: Control Signal Table (Contd.)

- Signals are defined on a register basis
- LOADQ and LOADB: external signals controlled from the system using the multiplier and will not be considered a part of this design
- Many control signals are "reused" for different registers.
 - These 4 control signals are the "outputs" of the control unit: initialize, load, shift_dec, clear_c

6

Multiplier Example - Sequencing Part of ASM

 - With the outputs represented by the table, they can be removed from the ASM making the ASM to represent only the sequencing (next state) behavior



Similar to FSM →

7

Hardwired Control

- Control Design Methods
 - Procedure specializations that use a single signal to represent each state
 - Sequence Register and Decoder
 - Sequence register with encoded states, e.g., 00, 01, 10, 11.
 - Decoder outputs produce "state" signals, e.g., 0001, 0010, 0100, 1000.
 - One Flip-flop per State
 - Flip-flop outputs as "state" signals, e.g., 0001, 0010, 0100, 1000.

8

Multiplier Example: Sequencer and Decoder Design - Specification

- Initially, use sequential circuit design techniques
- First, define:
 - States: IDLE, MUL0, MUL1
 - Input Signals: G, Z, Q_0 (Q_0 affects outputs, not next state)
 - Output Signals: Initialize, LOAD, Shift_Dec, Clear_C
 - State Transition Diagram (Use Sequencing ASM)
 - Output Function: Use Control Signal Table
- Second, find
 - State Assignments
 - Use two state bits to encode the three states IDLE, MUL0, and MUL1.

State	M1	M0
IDLE	0	0
MUL0	0	1
MUL1	1	0
Unused	1	1

9

Multiplier Example: Sequencer and Decoder Design - Formulation

- Assuming that state variables M1 and M0 are decoded into states, the next state part of the state table is:

Current State	Input G Z	Next State M1 M0
IDLE	0 0	0 0
IDLE	0 1	0 0
IDLE	1 0	0 1
IDLE	1 1	0 1
MUL0	0 0	1 0
MUL0	0 1	1 0
MUL0	1 0	1 0
MUL0	1 1	1 0

Current State	Input G Z	Next State M1 M0
MUL1	0 0	0 1
MUL1	0 1	0 0
MUL1	1 0	0 1
MUL1	1 1	0 0
Unused	0 0	d d
Unused	0 1	d d
Unused	1 0	d d
Unused	1 1	d d


10

Multiplier Example: Sequencer and Decoder Design –Equations Derivation/Optimization

- Finding the equations for M1 and M0 using decoded states:
 - $M1 = MUL0$
 - $M0 = IDLE \cdot G + MUL1 \cdot \bar{Z}$
- The output equations using the decoded states:
 - Initialize = IDLE · G
 - Load = MUL0 · Q_0
 - Clear_C = IDLE · G + MUL1
 - Shift_dec = MUL1
- Doing multiple level optimization, extract IDLE · G:
 - START = IDLE · G
 - $M1 = MUL0$
 - $M0 = START + MUL1 \cdot \bar{Z}$
 - Initialize = START
 - Load = MUL0 · Q_0
 - Clear_C = START + MUL1
 - Shift_dec = MUL1
- The resulting circuit using flip-flops, a decoder, and the above equations is given on the next slide.

11

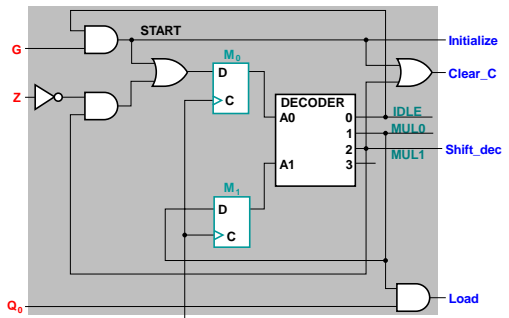Multiplier Example: Sequencer and Decoder Design - Implementation



12

```

--Binary multiplier with n=4
library ieee;
use ieee.std_logic_unsigned.all;
entity binary_multiplier is
port(CLK, RESET, G, LOADB, LOADQ: in std_logic;
MULT_IN : in std_logic_vector (3 downto 0);
MULT_OUT : out std_logic_vector (7 downto 0));
end entity binary_multiplier;

architecture behavior_4 of binary_multiplier is
type state_type is (IDLE, MUL0, MUL1);
variable P:=3;
signal state, next_state : state_type;
signal A, B, Q:std_logic_vector(3 downto 0);
signal C, Z:std_logic;
begin
Z<= P(1) NOR R(0);
MULT_OUT<= A & Q;

state_register : process (CLK, RESET)
begin
if (RESET = '1') then
state <= IDLE;
else if (CLK'event and CLK='1') then
state <= next_state;
end if;
end process;

next_state_func : process (G, Z, state)
begin
case state is
when IDLE =>
when G='1' then next_state <= MUL0;
else next_state <= IDLE;
end if;
when MUL0 =>
next_state <= MUL1;
when MUL1 =>
if Z='1' then
next_state <= IDLE;
else
next_state <= MUL0;
end if;
end case;
end process;
end behavior_4;

```

```

datapath_func : process (CLK)
variable CA : std_logic_vector (4 downto 0);
begin
if (CLK'event and CLK='1') then
if LOADB='1' then
B <= MULT_IN;
end if;
if LOADQ='1' then
Q <= MULT_IN;
end if;
case state is
when IDLE =>
if G = '1' then
C <= '0';
A <= "0000";
P <= "11";
end if;
when MUL0 =>
if Q(0) = '1' then
CA := ('0' & A) + ('0' & B);
else
CA := C & A;
end if;
C <= CA(4);
A <= CA(3 downto 0);
when MUL1 =>
C <= '0';
A <= C & A(3 downto 1);
Q <= A(0) & Q(3 downto 1);
P <= P - '01';
end case;
end if;
end process;
end datapath_func;

```

Speeding Up the Multiplier


- In processing each bit of the multiplier, the circuit visits states MUL0 and MUL1 in sequence.
- By redesigning the multiplier, is it possible to visit only a single state per bit processed?

Speeding Up Multiply (Contd.)

- The operations in MUL0 and MUL1:
 - In MUL0, a conditional add of B
 - In MUL1, a right shift of C || A || Q in a shift register, the decrementing of P, and a test for P = 0 (on the old value of P)
- Any solution that uses one state must combine all of the operations listed into one state
 - The operations involving P are already done in a single state, so not a problem.
 - The right shift, however, depends on the result of the conditional addition. So these two operations must be combined!

Speeding Up Multiply (Contd.)

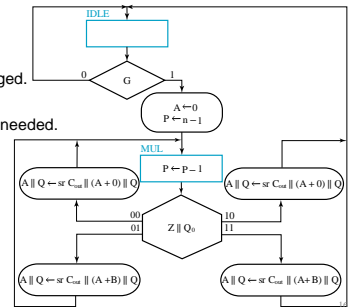- By replacing the shift register with a combinational shifter and combining the adder and shifter, the states can be merged.
- The C-bit is no longer needed.
- In this case, Z and Q₀ have been made into a vector.



Microprogrammed Control

- **Microprogrammed Control** — a control unit with binary control values stored as words in memory.
- **Microinstructions** — words in the control memory.
- **Microprogram** — a sequence of microinstructions.
- **Control Memory** — RAM or ROM memory holding the microinstructions.
 - **Writable Control Memory** — RAM Memory into which microinstructions may be written

