

## ECE 3401 Lecture 16

### Memory & Timing Issues

## Memories Overview

- **Memories**
  - Memory categories and timing
  - Random access memory (RAM):
    - SRAM
    - DRAM
- Timing issues
  - Sequential system timing requirements
  - Clock skew and clock jitter
  - Clock distribution


## Memories

Read-Write Memory		Read-Only Memory	
Volatile Memory		Non-volatile Memory	
Random Access	Sequential Access	Mask-Programmed ROM (PROM) (nonvolatile)	
DRAM	FIFO LIFO Shift Register CAM	EPROM	
SRAM		EEPROM	
		FLASH	

- Volatile: need electrical power
- Nonvolatile: magnetic disk, retains its stored information after the removal of power
- Random access: memory locations can be read or written in a random order
- EPROM: erasable programmable read-only memory
- EEPROM: electrically erasable programmable read-only memory
- FLASH: memory stick, USB disk
- Access pattern: sequential access: (video memory streaming) first-in-first-out (buffer), last-in-first-out (stack), shift register, content-addressable memory

 
## Memories

- $k$  address lines are decoded to address  $2^k$  words of memory.
- Each word is  $n$  bits.
- Read and Write are single control lines defining the simplest memory operations.



 
## Memory Operation Timing - Reading

- Most basic memories are asynchronous
  - Storage in latches or storage of electrical charge
  - No clock
  - Controlled by control inputs and address, which are controlled by CPU and synchronized by its own clock
- Timing of signal changes/data observation is critical to the operation



- Read cycle: the access time, the maximum time from the application of the address to the appearance of the data at the Data output.

## Memory Operation Timing - Writing

 

- Write cycle: the maximum time from the application of the address to the completion of all internal operations required to store a word
- Critical times measured with respect to edges of write pulse (1-0-1):
  - Address must be established at least a specified time before 1-0 and held for at least a specified time after 0-1 to avoid disturbing stored contents of other addresses
  - Data must be established at least a specified time before 0-1 and held for at least a specified time after 0-1 to write correctly

## VHDL code for ROM

```

library IEEE;
use IEEE.std_logic_1164.all;

ENTITY rom8x4 IS
PORT (
addr: in std_logic_vector(2 downto 0);
q: out std_logic_vector(3 downto 0);
END rom8x4;

ARCHITECTURE behav OF rom8x4 IS
BEGIN
PROCESS(addr)
BEGIN
CASE addr IS
when "000" => q <= "0001";
when "001" => q <= "0000";
when "010" => q <= "0111";
when "011" => q <= "1101";
when "100" => q <= "1000";
when "101" => q <= "1100";
when "110" => q <= "0110";
when "111" => q <= "1011";
when others => NULL;
END case;
END process;
END behav;

```

7

## ROMS in Xilinx library

- ROM16x1 (16-word by 1 bit ROM)
- ROM32x1
- ROM64x1
- ROM128x1
- ROM256x1

8


## ROMS in Xilinx library

```

component ROM16X1
-- synthesis translate_off
generic (INIT : bit_vector := X"0016");
-- synthesis translate_on
port (O : out STD_ULOGIC;
A0 : in STD_ULOGIC;
A1 : in STD_ULOGIC;
A2 : in STD_ULOGIC;
A3 : in STD_ULOGIC);
end component;

architecture beh of rom is
begin
ROM16X1_INSTANCE_NAME : ROM16X1
-- synthesis translate_off
generic map (INIT => hex_value )
-- synthesis translate_on
port map (O => user_O, A0 => user_A0, A1 => user_A1,
A2 => user_A2, A3 => user_A3 );
end architecture

```

 

9

## How do we use ROM

- VHDL components in a VHDL design
- Graphical components in a schematic

```

architecture beh of proc is
signal ABUS : std_logic_vector(3 downto 0);
signal DBUS : std_logic_vector(1 downto 0);
begin
bit0 : ROM16X1
-- synthesis translate_off
generic map (INIT => "1010 1110 0001 0001")
-- synthesis translate_on
port map (O => DBUS(0), A0 => ABUS(0),
A1 => ABUS(1), A2 => ABUS(2), A3 => ABUS(3) );
bit1 : ROM16X1
-- synthesis translate_off
generic map (INIT => "1101 1010 1111 0101")
-- synthesis translate_on
port map (O => DBUS(1), A0 => ABUS(0),
A1 => ABUS(1), A2 => ABUS(2), A3 => ABUS(3) );
rom_inc : process(CLK) is
begin
if (CLK'event and CLK='1') then
ABUS <= ABUS + 1;
end if;
end process;
jump : process(DBUS) is
begin
if (DBUS="11") then
ABUS <= "0000";
end if;
end;
end architecture

```

10

## Random Access Memories (RAMs)

- Read/Write memory
- Types:
  - Static RAM (SRAM):
    - Once a word is written at a location, it remains stored as long as power is applied to the chip, unless the same location is written again.
    - Fast speed, but their cost per bit higher.
    - Application: Caches memories in Microprocessor
  - Dynamic RAM (DRAM):
    - The data stored at each location must be periodically refreshed by reading it and then writing it back again, otherwise it disappears.
    - Their density is greater and their cost per bit lower, but the speed is slower.

11

## RAMS in Xilinx library

- Static Block RAMs
- Single port
  - RAMB4\_S1, RAMB4\_S2, RAMB4\_S8, RAMB4\_S16
- Dual port
  - RAMB4\_S1\_S1, RAMB4\_S1\_S2, ... RAMB4\_S16\_S16
- The difference between single port RAM and dual port RAM is that single port RAM can be accessed at one address at one time, thus you can read/write only one memory cell during each clock cycle. Dual port RAM has ability to simultaneously read and write different memory cells at different addresses.
- SPRAM uses a 6 transistor basic ram cell, while the dual port ram cell uses 8 transistor cell for memory.

12

## RAMS in Xilinx library

```


component RAMB4_S1
-- synthesis translate_off
generic (INIT_00 : bit_vector :=
X"0000000000000000000000000000000000000000000000000000000000000000";
INIT_01 : bit_vector :=
X"0000000000000000000000000000000000000000000000000000000000000000";
...
);
-- synthesis translate_on
port (DO : out STD_LOGIC_VECTOR (0 downto 0);
ADDR : in STD_LOGIC_VECTOR (11 downto 0);
CLK : in STD_ULOGIC;
DI : in STD_LOGIC_VECTOR (0 downto 0);
EN : in STD_ULOGIC;
RST : in STD_ULOGIC;
WE : in STD_ULOGIC);
end component;

RAMB4_Sn_INSTANCE_NAME: RAMB4_Sn
-- synthesis translate_off
generic map (INIT_00 => 64bit_hex_value,
INIT_01 => 64bit_hex_value,
INIT_0F => 64bit_hex_value)
-- synthesis translate_on
port map (DO => user_DO, ADDR => user_ADDR, CLK => user_CLK, DI => user_DI,
EN => user_EN, RST => user_RST, WE => user_WE);
    
```


13
 
## SRAM Cell

- Array of storage cells used to implement static RAM



 - Storage Cell
  - SR Latch
  - Input "Select" for control
  - Dual Rail Data
    - Inputs B and  $\bar{B}$
    - Outputs C and  $\bar{C}$




14
 
## SRAM Bit Slice

- Represents all circuitry that is required for  $2^n$  1-bit words

- Multiple RAM cells
  - Control Lines:
    - Word select  $i$  — one for each word
    - Read/Write
    - Bit Select
  - Data Lines:
    - Data in
    - Data out




15
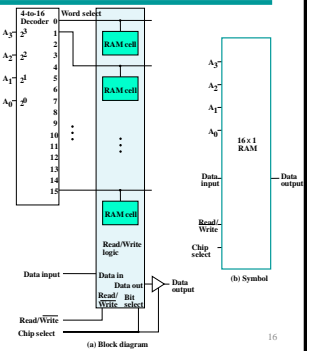
## $2^n$ -Word by 1-Bit RAM IC

- To build a RAM IC from a RAM slice:

- Decoder decodes the  $n$  address lines to  $2^n$  word select lines
- A 3-state buffer on the data output permits RAM ICs to be combined into a RAM with  $c \times 2^n$  words



16


## Cell Arrays and Coincident Selection

- Memory arrays can be very large =>
  - Large decoders
  - Large fanouts for the input bit lines
  - The decoder size and fanouts can be reduced by approximately  $\sqrt{n}$  using a coincident selection in a 2-D array: uses two decoders, one for words and one for bits:
    - Word select becomes Row select
    - Bit select becomes Column select
- See next slide for example

17
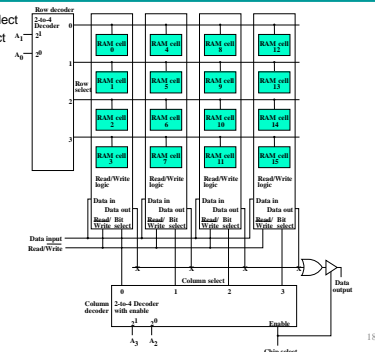
## Cell Arrays and Coincident Selection (Contd.)


$A_1$  and  $A_0$  used for Row select  
 $A_3$  and  $A_2$  for Column select



18
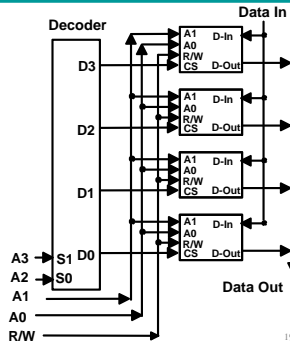
## Making Larger Memories


- We can make larger memories from smaller ones by using the decoded higher order address bits to control CS (chip select) lines, tying all address, data, and R/W lines in parallel.
- A 16-Word by 1-Bit memory constructed using 4-Word by 1-Bit memory.



19
 
## Making Wider Memories

- Tie the address and control lines in parallel and keep the data lines separate.
- Example: make a 4-word by 4-bit memory from 4, 4-word by 1-bit memories
- Note: Both 16x1 and 4x4 memories take 4-chips and hold 16 bits of data.




## DRAM

- Basic Principle: Storage of information on capacitors.
- Charge and discharge of capacitor to change stored value
- Use of transistor as "switch" to:
  - Store charges
  - Charge or discharge

21
 
## Dynamic RAM (Contd.)


- Circuit, hydraulic analogy, and logical model.



22
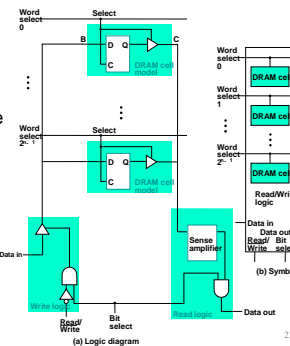
## Dynamic RAM - Bit Slice

- C driven by 3-state drivers
- Sense amplifier is used to change the small voltage change on C into H or L
- In the electronics, B, C, and the sense amplifier output are connected to make destructive read into non-destructive read



23