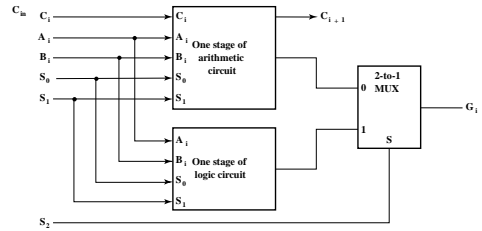


ECE 3401 Lecture 18

Microprogramming (I)

Arithmetic Logic Unit (ALU)

- Decompose the ALU into:
 - An arithmetic circuit & A logic circuit
 - A selector to pick between the two circuits




Arithmetic Circuit Design


- Arithmetic circuit design
 - Decompose the arithmetic circuit into:
 - An n-bit parallel adder
 - A block of logic that selects four choices for the B input to the adder

- There are only four functions of B to select as Y in $G = A + Y + C_{in}$:

$C_{in} = 0$	$C_{in} = 1$
0	$G = A + 1$
B	$G = A + B$
\bar{B}	$G = A + \bar{B} + 1$
1	$G = A - 1$
	$G = A$

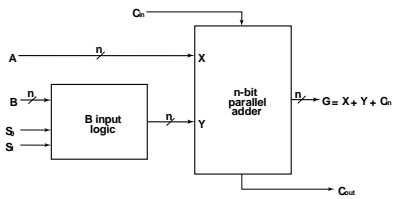


4-Bit Basic Left/Right Shifter

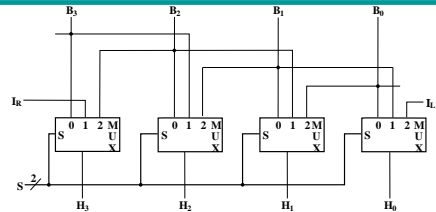


- Serial Inputs:
 - I_R for right shift
 - I_L for left shift
- Shift Functions:
 - $(S_1, S_0) = 00$ Pass B unchanged
 - 01 Right shift
 - 10 Left shift
 - 11 Unused

Barrel Shifter

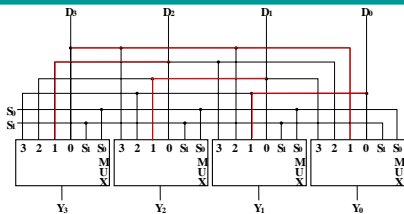


- A rotate is a shift in which the bits shifted out are inserted into the positions vacated
- The circuit rotates its contents left from 0 to 3 positions depending on S:
 - S = 00 position unchanged
 - S = 01 rotate left by 1 positions
 - S = 10 rotate left by 2 positions
 - S = 11 rotate left by 3 positions

Combinational Shifter from MUXes

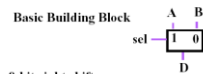

- Example 8-bit:
 - Layer 1 shifts by 0, 4
 - Layer 2 shifts by 0, 2
 - Layer 3 shifts by 0, 1


8-bit right shifter

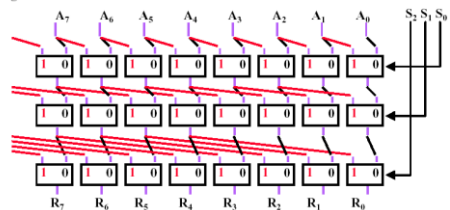


- Large barrel shifters can be constructed using:
 - Layers of multiplexers
 - 2 - dimensional array circuits designed at the electronic level

Datapath Representation

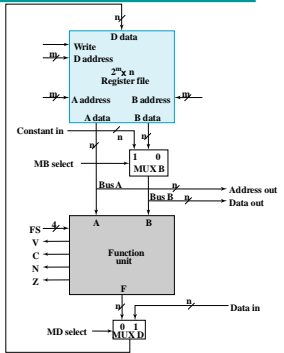- In the register file:
 - Select inputs for multiplexers => A address & B address
 - Decoder input => D address
 - Load enable => write
 - Input data to the registers => D data
 - Multiplexer outputs => A data & B data
- The register file now appears like a memory based on clocked flip-flops
- FS?



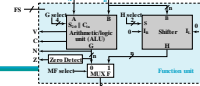Definition of Function Unit Select (FS) Codes



FS(3:0)	MF Select	G Select(3:0)	H Select(1:0)	Microoperation
0000	0	0000	XX	$F \leftarrow A$
0001	0	0001	XX	$F \leftarrow A + 1$
0010	0	0010	XX	$F \leftarrow A + B$
0011	0	0011	XX	$F \leftarrow A + B + 1$
0100	0	0100	XX	$F \leftarrow A + \bar{B}$
0101	0	0101	XX	$F \leftarrow A + \bar{B} + 1$
0110	0	0110	XX	$F \leftarrow A - 1$
0111	0	0111	XX	$F \leftarrow A$
1000	0	1X00	XX	$F \leftarrow A \wedge B$
1001	0	1X01	XX	$F \leftarrow A \vee B$
1010	0	1X10	XX	$F \leftarrow A \oplus B$
1011	0	1X11	XX	$F \leftarrow \bar{A}$
1100	1	XXXX	00	$F \leftarrow B$
1101	1	XXXX	01	$F \leftarrow sr B$
1110	1	XXXX	10	$F \leftarrow sl B$

Boolean Equations:
 $MFS = F_3 F_2$
 $GS_i = F_i$
 $HS_i = F_i$


The Control Word

- The datapath has many control input signals, can be organized into a *control word*
- To execute a microinstruction, we apply control word values for a clock cycle.

15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
DA	AA	BA	MB	FS	MD	RW									

Control word

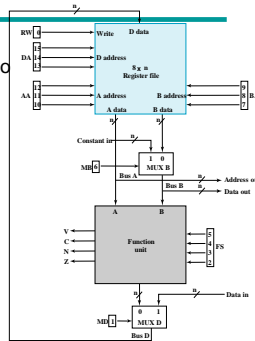DA – D Address, AA – A Address
 BA – B Address, MB – Mux B
 FS – Function Select, MD – Mux D
 RW – Register Write



Control Word Encoding

DA, AA, BA	MB	FS	MD	RW		
Function Code	Function Code	Function Code	Function Code	Function Code		
R0	000	Register 0	$F \leftarrow A$	0000	Function 0	No write 0
R1	001	Constant 1	$F \leftarrow A + 1$	0001	Data In 1	Write 1
R2	010	—	$F \leftarrow A + B$	0010	—	—
R3	011	—	$F \leftarrow A + B + 1$	0011	—	—
R4	100	—	$F \leftarrow A + \bar{B}$	0100	—	—
R5	101	—	$F \leftarrow A + \bar{B} + 1$	0101	—	—
R6	110	—	$F \leftarrow A - 1$	0110	—	—
R7	111	—	$F \leftarrow A$	0111	—	—
			$F \leftarrow A \wedge B$	1000	—	—
			$F \leftarrow A \vee B$	1001	—	—
			$F \leftarrow A \oplus B$	1010	—	—
			$F \leftarrow \bar{A}$	1011	—	—
			$F \leftarrow B$	1100	—	—
			$F \leftarrow sr B$	1101	—	—
			$F \leftarrow sl B$	1110	—	—

Microoperations for the Datapath – Symbolic & Binary Representation

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	R1	R2	R3	Register	$F = A + \bar{B} + 1$	Function Write	
$R4 \leftarrow sl R6$	R4	—	R6	Register	$F = sl B$	Function Write	
$R7 \leftarrow R7 + 1$	R7	R7	—	Register	$F = A + 1$	Function Write	
$R1 \leftarrow R0 + 2$	R1	R0	—	Constant	$F = A + B$	Function Write	
Data out $\leftarrow R3$	—	—	R3	Register	—	—	No Write
$R4 \leftarrow$ Data in	R4	—	—	—	—	Data in	Write
$R5 \leftarrow 0$	R5	R0	R0	Register	$F = A \oplus B$	Function Write	

Micro-operation	DA	AA	BA	MB	FS	MD	RW
$R1 \leftarrow R2 - R3$	001	010	011	0	0101	0	1
$R4 \leftarrow sl R6$	100	XXX	110	0	1110	0	1
$R7 \leftarrow R7 + 1$	111	111	XXX	0	0001	0	1
$R1 \leftarrow R0 + 2$	001	000	XXX	1	0010	0	1
Data out $\leftarrow R3$	XXX	XXX	011	0	XXXX	X	0
$R4 \leftarrow$ Data in	100	XXX	XXX	X	XXXX	1	1
$R5 \leftarrow 0$	101	000	000	0	1010	0	1

Datapath Simulation

