

## ECE 3401 Lecture 20

### Microprogramming (III)

## Overview



- Part 1 – Datapaths
  - Introduction
  - Datapath Example
  - Datapath Representation and Control Word
- Part 2 – A Simple Computer
  - Instruction Set Architecture (ISA)
  - Single-Cycle Hardwired Control
    - PC Function
    - Instruction Decoder
    - Example Instruction Execution
- Part 3 – Multiple Cycle Hardwired Control
  - Single Cycle Computer Issues
  - Sequential Control Design

## Single-Cycle Computer Issues

- Shortcoming of Single Cycle Design
  - Complexity of instructions executable in a single cycle is limited
  - Accessing both an instruction and data from a simple single memory impossible
  - A long worst case delay path limits clock frequency and the rate of performing instructions
- Handling of Shortcomings
  - The first two shortcomings can be handled by the multiple-cycle computer
  - The third shortcoming is dealt with by using a technique called pipelining described in later lectures
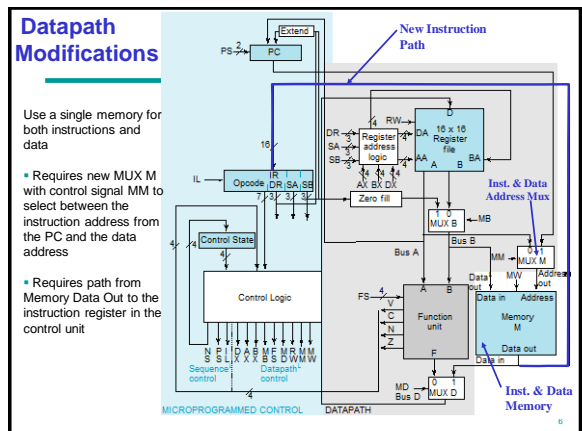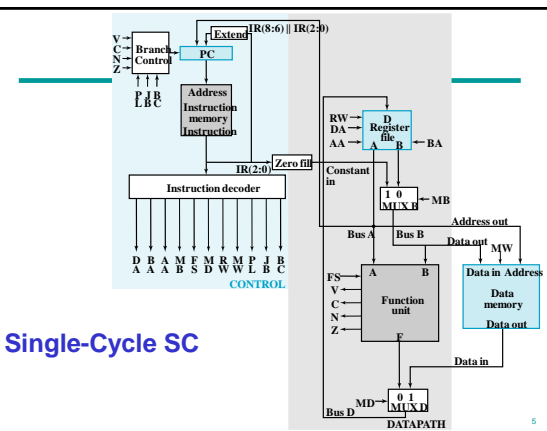
## Multiple-Cycle Computer


- Converting the single-cycle computer into a multiple-cycle computer involves:
  - Modifications to the datapath/memory
  - Modification to the control unit
  - Design of a multiple-cycle hardwired control



## Datapath Modifications (Continued)

- Additional registers needed to hold operands between cycles
  - Add 8 temporary storage registers to the Register File
    - Register File becomes 16 x 16
    - Addresses to Register File increase from 3 to 4 bits
  - Register File addresses come from:
    - The instruction for the Storage Resource registers (0 to 7)
    - The control word for the Temporary Storage registers (8 to 15)
  - Add Register Address Logic to the Register File to select the register address sources
    - Three new control fields for register address source selection and temporary storage addressing: DX, AX, BX


7

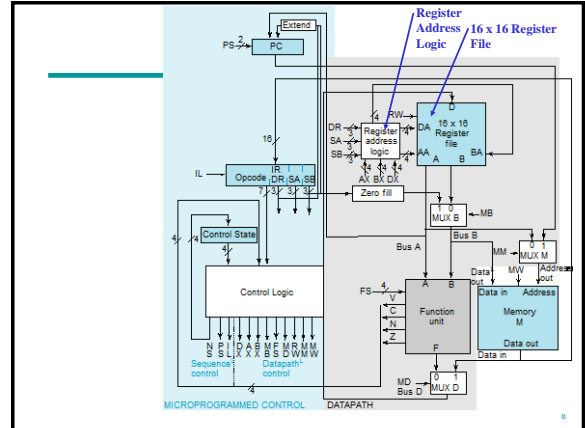

## Control Unit Modifications

- Must hold instruction over the multiple cycles to draw on instruction information throughout instruction execution
  - Requires an Instruction Register (IR) to hold the instruction
    - Load control signal IL
  - Requires the addition of a "hold" operation to the PC since it only counts up to obtain a new instruction
    - New encoding for the PC operations uses 2 bits

9

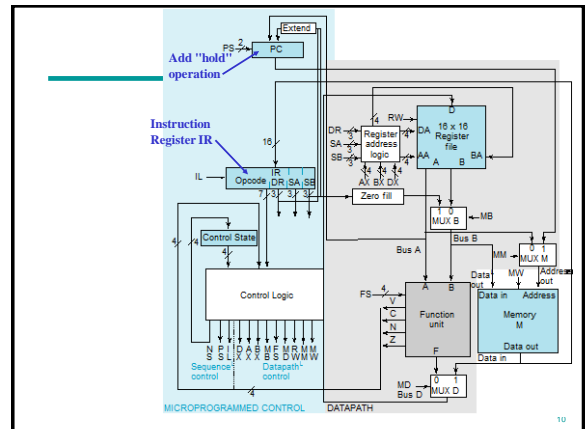


10

## Sequential Control Design


- To control microoperations over multiple cycles, a Sequential Control replaces the Instruction Decoder
  - Input: Opcode, Status Bits, Control State
  - Output:
    - Control Word (Modified Datapath Control part)
    - Next State: Control Word (New Sequencing Control part)
  - Consists of:
    - Register to store the Control State
    - Combinational Logic to generate the Control Word (both sequencing and datapath control parts)
  - The Combinational Logic is quite complex so we assume that it is implemented by using a PLA or synthesized logic and focus on ASM level design

11

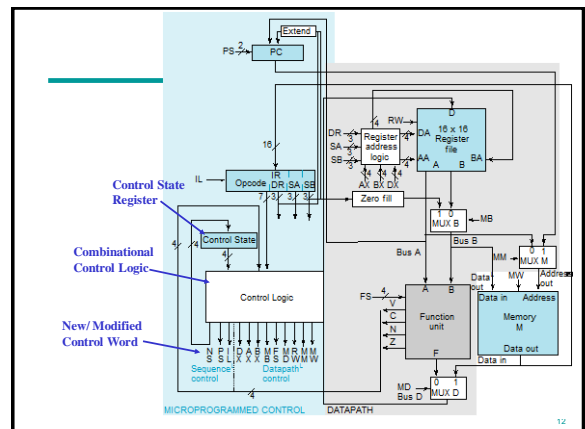

12

## Control Word

 

- Datapath part: field MM added, and fields DX, AX, and BX replace DA, AA, and BA, respectively
  - If the MSB of a field is 0, e.g., AX = 0XXX, then AA is 0 concatenated with SA (3bits) field in the IR
  - If the MSB of a field is 1, e.g. AX = 1011, then AA = 1011
- Sequencing part:
  - IL controls the loading of the IR
  - PS controls the operations of the PC
  - NS gives the next state of the Control State register
    - E.g., NS is 4 bits, the length of the Control State register - 16 states are viewed as adequate for this design

13

## Encoding for Datapath Control

DX	AX	BX	Code	MB	Code	FS	Code	MD	RW	MM	MW	Code
R[DR]	R[SA]	R[SB]	0XXX	Register	0	$F \leftarrow A$	0000	FnUt	No write	Address	No write	0
R8	R8	R8	1000	Constant	1	$F \leftarrow A + 1$	0001	Data In	Write	PC	Write	1
R9	R9	R9	1001			$F \leftarrow A + B$	0010					
R10	R10	R10	1010			Unused	0011					
R11	R11	R11	1011			Unused	0100					
R12	R12	R12	1100			$F \leftarrow A + \bar{B} + 1$	0101					
R13	R13	R13	1101			$F \leftarrow A - 1$	0110					
R14	R14	R14	1110			Unused	0111					
R15	R15	R15	1111			$F \leftarrow A \wedge B$	1000					
						$F \leftarrow A \vee B$	1001					
						$F \leftarrow A \oplus B$	1010					
						$F \leftarrow \bar{A}$	1011					
						$F \leftarrow B$	1100					
						$F \leftarrow s_r B$	1101					
						$F \leftarrow s_l B$	1110					
						Unused	1111					

14

## Encoding for Sequencing Control

	NS		PS		IL	
	Next State	Action	Code	Action	Code	
Gives next state of Control State Register	Hold PC	00	No load	0		
	Inc PC	01	Load instr.	1		
	Branch	10				
	Jump	11				

15

## ASM Charts for Sequential Control

- An instruction requires two steps:
  - Instruction fetch* – obtaining an instruction from memory
  - Instruction execution* – the execution of a sequence of microoperations to perform instruction processing
  - Due to the use of the IR, these two steps require a minimum of **two clock cycles**
- ISA: Instruction Specifications and ASM charts for the instructions (that all require two clock cycles)
  - A vector decision box is used for the opcode
  - Scalar decision boxes are used for the status bits

16


## ISA: Instruction Specifications (for reference)

### Instruction Specifications for the Simple Computer - Part 1

Instruction	Opcode	Mnemonic	Format	Description	Status Bits
Move A	0000000	MOVA	RD,RA	$R[DR] \leftarrow R[SA]$	N, Z
Increment	0000001	INC	R,D,RA	$R[DR] \leftarrow R[SA] + 1$	N, Z
Add	0000010	ADD	R,D,RA,RB	$R[DR] \leftarrow R[SA] + R[SB]$	N, Z
Subtract	0000101	SUB	R,D,RA,RB	$R[DR] \leftarrow R[SA] - R[SB]$	N, Z
Decrement	0000110	DEC	R,D,RA	$R[DR] \leftarrow R[SA] - 1$	N, Z
AND	0001000	AND	R,D,RA,RB	$R[DR] \leftarrow R[SA] \wedge R[SB]$	N, Z
OR	0001001	OR	R,D,RA,RB	$R[DR] \leftarrow R[SA] \vee R[SB]$	N, Z
Exclusive OR	0001010	XOR	R,D,RA,RB	$R[DR] \leftarrow R[SA] \oplus R[SB]$	N, Z
NOT	0001011	NOT	R,D,RA	$R[DR] \leftarrow \bar{R[SA]}$	N, Z

17
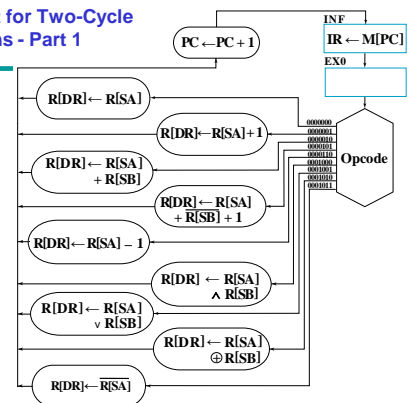
## ASM Chart for Two-Cycle Instructions - Part 1



18

## ISA: Instruction Specifications (for reference)


### Instruction Specifications for the Simple Computer - Part 2

Instruction	Opcode	Mnemonic	Format	Description	Status Bits
Move B	0001100	MOVB	RD,RB	R[DR] ← R[SB]	
Shift Right	0001101	SHR	RD,RB	R[DR] ← sr R[SB]	
Shift Left	0001110	SHL	RD,RB	R[DR] ← sl R[SB]	
Load Immediate	1001100	LDI	RD,OP	R[DR] ← zf OP	
Add Immediate	1000010	ADI	RD,RA,OP	R[DR] ← R[SA] + zf OP	
Load	0010000	LD	RD,RA	R[DR] ← M[SA]	
Store	0100000	ST	RA,RB	M[SA] ← R[SB]	
Branch on Zero	1100000	BRZ	R.A,AD	if (R[SA] = 0) PC ← PC + se AD	
Branch on Negative	1100001	BRN	R.A,AD	if (R[SA] < 0) PC ← PC + se AD	
Jump	1110000	JMP	RA	PC ← R[SA]	

19
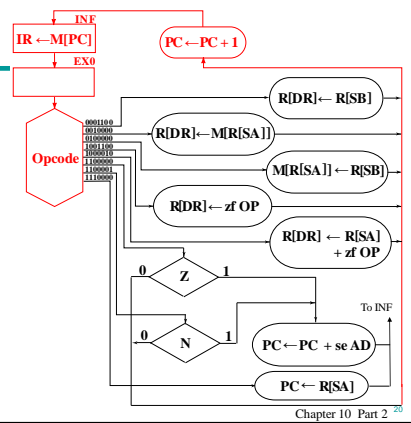
## ASM Chart for 2-Cycle Instructions - Part 2

- Portion in Red duplicated from previous ASM chart



Chapter 10 Part 2

## State Table for 2-Cycle Instructions

State	Inputs		Next state	Outputs												Comments
	Opcode	VCNZ		I L S	I P	D X	A X	B X	B	F S	M D	R M	M M	M W		
INF	XXXXXX	XXXX	EXO	1	00	XXXX	XXXX	XXXX	X	XXXX	X	0	1	0		IR ← M[PC]
EXO	0000000	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	0000	0	1	X	0		MOVB R[DR] ← R[SA]*
EXO	0000001	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	0001	0	1	X	0		JNC R[DR] ← R[SA] + 1*
EXO	0000010	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	0010	0	1	X	0		ADD R[DR] ← R[SA] + R[SB]*
EXO	0000101	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	0101	0	1	X	0		SUB R[DR] ← R[SA] + R[SB]* + 1*
EXO	0001110	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	0110	0	1	X	0		DEC R[DR] ← R[SA] + (-1)*
EXO	0010000	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	1000	0	1	X	0		AND R[DR] ← R[SA] & R[SB]*
EXO	0010001	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	1001	0	1	X	0		OR R[DR] ← R[SA] ∨ R[SB]*
EXO	0010010	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	1010	0	1	X	0		XOR R[DR] ← R[SA] ⊗ R[SB]*
EXO	0010101	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	1011	0	1	X	0		NOT R[DR] ← R[SA]*
EXO	001100	XXXX	INF	0	01	0XXX	XXXX	XXXX	X	1100	0	1	X	0		MOVB R[DR] ← R[SB]*
EXO	0010000	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	XXXX	1	1	0	0		LD R[DR] ← M[R[SA]]*
EXO	0100000	XXXX	INF	0	01	XXXX	0XXX	XXXX	X	0	0	0	0	0		ST M[R[SA]] ← R[SB]*
EXO	1001100	XXXX	INF	0	01	0XXX	XXXX	XXXX	X	1100	0	1	0	0		LDI R[DR] ← zf OP*
EXO	1000010	XXXX	INF	0	01	0XXX	0XXX	XXXX	X	0010	0	1	0	0		ADI R[DR] ← R[SA] + zf OP*
EXO	1100000	XXXX	INF	0	10	XXXX	0XXX	XXXX	X	0000	X	0	0	0		BRZ PC ← PC + se AD
EXO	1100000	XXXX	INF	0	01	XXXX	0XXX	XXXX	X	0000	X	0	0	0		BRZ PC ← PC + 1
EXO	1100001	XXXX	INF	0	10	XXXX	0XXX	XXXX	X	0000	X	0	0	0		BRN PC ← PC + se AD
EXO	1100001	XXXX	INF	0	01	XXXX	0XXX	XXXX	X	0000	X	0	0	0		BRN PC ← PC + 1
EXO	1110000	XXXX	INF	0	11	XXXX	0XXX	XXXX	X	0000	X	0	0	0		JMP PC ← R[SA]

\* For this state and input combinations, PC ← PC+1 also occurs

21

## 3-Process ASM VHDL Code

entity controller is

```

Port ( opcode : in std_logic_vector(6 downto 0);
      reset, clk : in std_logic;
      zero, negative : in std_logic;
      IL, MB, MD, MM, RW, MW : out std_logic;
      PS : out std_logic_vector(1 downto 0);
      DX, AX, BX, FS : out std_logic_vector(3 downto 0) );

```

end controller;

architecture Behavioral of controller is

```

type state_type is (RES, FTH, EX);
signal cur_state, next_state : state_type;
begin
state_registerprocess(clk, reset)
begin
if(reset='1') then
cur_state<=RES;
else if clk'event and clk='1' then
cur_state<=next_state;
end if;
end process;
end architecture;

```

22

## 3-Process ASM VHDL Code

```


out_func: process (cur_state, opcode, zero, negative)
begin
(IL,PS, MB, FS, MD, RW, MM, MW) <= std_logic_vector(0x"000");
FS<="0000";
case cur_state is
when RES =>
next_state <= FTH;
when FTH =>
-- set the control vector values
next_state <= EXE;
when EXE =>
case opcode is
when "0000000" =>
end process;
End Behavioral;

```

23
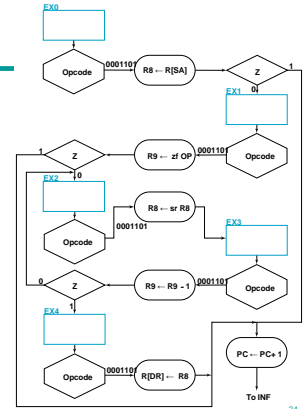
## ASM Chart for Multiple Bits Right Shift

- R8 – used to perform shifts
- R9 – used to store and decrement shift count
- Zero test in EX1 is to determine if the shift amount is 0; if so, goes to state INF



24

## State Table For Multiple Bits Right Shift

State	Inputs		Next state	Outputs													Comments
	Opcode	VCNZ		L	PS	DX	AN	RN	MB	FS	MD	RW	MM	M	W		
EX0	0001101	XXX0	EX1	0	00	1000	0XXX	XXXX	X	0000	0	1	X	0	SRM	R8 ← R(SA); Z <sub>7</sub> ← EX1	
EX0	0001101	XXX1	INF	0	01	1000	0XXX	XXXX	X	0000	0	1	X	0	SRM	R8 ← R(SA); Z <sub>7</sub> ← INF <sup>9</sup>	
EX1	0001101	XXX0	EX2	0	00	1001	XXXX	XXXX	1	1100	0	1	X	0	SRM	R9 ← Z(OP); Z <sub>7</sub> ← EX2	
EX1	0001101	XXX1	INF	0	01	1001	XXXX	XXXX	1	1100	0	1	X	0	SRM	R9 ← Z(OP); Z <sub>7</sub> ← INF <sup>9</sup>	
EX2	0001101	XXX0	EX3	0	00	1000	XXXX	1000	0	1101	0	1	X	0	SRM	R8 ← sr R8; Z <sub>7</sub> ← EX3	
EX2	0001101	XXX1	INF	0	01	1000	XXXX	1000	0	1101	0	1	X	0	SRM	R8 ← sr R8; Z <sub>7</sub> ← INF <sup>9</sup>	
EX3	0001101	XXX0	EX4	0	00	1001	1001	XXXX	X	0110	0	1	X	0	SRM	R9 ← R9 - 1; Z <sub>7</sub> ← EX4	
EX3	0001101	XXX1	INF	0	01	1001	1001	XXXX	X	0110	0	1	X	0	SRM	R9 ← R9 - 1; Z <sub>7</sub> ← INF <sup>9</sup>	
EX4	0001101	XXX0	INF	0	01	0XXX	1000	XXXX	X	0000	0	1	X	0	SRM	R(DR) ← R8; Z <sub>7</sub> ← INF <sup>9</sup>	

<sup>9</sup> For this state and input combinations, PC ← PC+1 also occurs