


## Topics

- CMOS Logic Delays
- Logical Effort

3 March 2009

1

## Multi-input Delay

 


3 March 2009

2

## Input Pattern Effects on Delay

### NAND

 


- Delay is dependent on the pattern of inputs (input combination)
  - delay is  $0.69 (R_p/2) C_L$
- **Low to high transition**
  - both inputs go low
    - delay is  $0.69 R_p C_L$
  - one input goes low
    - delay is  $0.69 R_p C_L$
- **High to low transition**
  - both inputs go high
    - delay is  $0.69 (2 R_n) C_L$

3 March 2009

3

## Delay Dependence on Input Patterns

 


3 March 2009

4

## Fan-In Considerations

4-input NAND gate

 

Propagation delay deteriorates rapidly as a function of fan-in – quadratically in the worst case.

- Gates with a fan-in greater than 4 should be avoided

3 March 2009

5

## CMOS Logic Gate Delays

- Using Logical Effort to simplify delay calculation
- Helps in deciding
  - Transistor sizing
  - Number of stages
  - Circuit Topology

3 March 2009

6

## Logical Effort

- Characterize process speed with delay parameter  $t_{p0}$ 
  - $d = d_{abc} / t_{p0}$
  - $t_{p0} \approx 20\text{ps}$  for a .25 micron process
- Process independent delay has two components
  - $d = p + h$
  - $h$  is the effort delay
  - $p$  is the parasitic delay

3 March 2009

7

## Logical Effort

- Effort delay has two components
  - $h = g * f$
  - $g$  is the logical effort
  - $f$  is the electrical effort or effective fanout
- Parasitic delay is the delay due to intrinsic delay of gate - mostly the drain capacitance
  - Independent of output load and sizing
  - Approximately equal to 1 for an inverter

3 March 2009

8

## Logical Effort

- Logical effort is a measure of the gate's ability to deliver current
  - An inverter has a logical effort of 1
  - Depends only on topology not on process or sizing
- Electrical effort is a measure of fanout
  - $C_{out} / C_{in}$

3 March 2009

9

## Logical Effort


- Logical Effort assignment
  - Ratio of the gate's input capacitance to the input capacitance of an inverter delivering the same amount of current
  - Can be derived through simulations and accurate measurement
  - Or through estimations based on transistor widths

3 March 2009

10

## Logical Effort

- Inverter

 

$$C_{in} = 3$$


$$g = \text{LogicalEffort} = 1$$

3 March 2009

11

## Logical Effort

- NAND

 

$$C_{in} = 4$$


$$g = \text{LogicalEffort} = 4/3$$

3 March 2009

12

## Logical Effort

- NOR

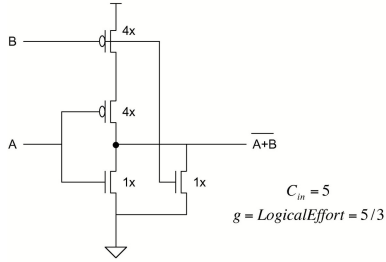


3 March 2009

13

## Logical Effort


- NOR

 

3 March 2009

14

## Logical Effort

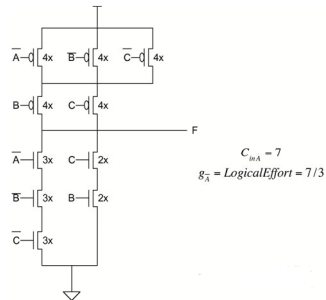

3 March 2009

15

## Logical Effort

Number of inputs	1	2	3	n
INV	1			
NAND		4/3	5/3	(n+2)/3
NOR		5/3	7/3	(2n+1)/3

3 March 2009

16

## Logical Effort

- Parasitic delay


Number of inputs	1	2	3	n
INV	$p_{inv}$			
NAND		$2 p_{inv}$	$3 p_{inv}$	$n p_{inv}$
NOR		$2 p_{inv}$	$3 p_{inv}$	$n p_{inv}$

3 March 2009

17

## Logical Effort

- Example: Inverter ring oscillator

 


- Estimate the frequency of the oscillator

3 March 2009

18

## Logical Effort

- Example: Inverter ring oscillator

 


- $g_i = 1$
- $f_i = 1$
- $p_i = 1$
- $d_i = g_i f_i + p_i = 2$

3 March 2009

19

## Logical Effort

- Example: Inverter ring oscillator

 


- Total delay =  $N \cdot d_i \cdot t_{p0} = 2N t_{p0}$
- Frequency =  $1/(4N t_{p0})$

3 March 2009

20

## Logical Effort

- Example: FO4 Inverter (Fanout of 4)

 


- $g_i = 1$
- $f_i = 4$
- $p_i = 1$
- $d_i = g_i f_i + p_i = 5$

3 March 2009

21

## Logical Effort

- Multistage logic networks

 


- Find path delay

3 March 2009

22

## Logical Effort

- Multistage logic networks

 

- Path Parasitic Delay

$$P = \sum P_i$$

- Path Delay

$$D = P + \sum g_i f_i$$

- How do we minimize D? How do we select the sizing?

3 March 2009

23

## Logical Effort

- Path effort is an indirect measure of the path delay

- Path Electrical Effort  $F = \frac{C_{out}}{C_{in}}$
- Path Logical Effort  $G = \prod g_i$
- Path Effort  $H = GF$

- The above does not include any consideration of the effect of fanout within the path


- H counts only the fanout of the output
- We need to express the branching behavior along the path

3 March 2009

24

## Logical Effort

- Branching Effort

 

$$b = \frac{C_{on-path} + C_{off-path}}{C_{on-path}} = \frac{C_{total}}{C_{useful}}$$

$$B = \prod b_i$$

$$FB = \frac{C_{out}}{C_{in}} \prod b_i = \prod f_i$$

3 March 2009

25

## Logical Effort

- Path Effort

$$H = G \times FB = \prod g_i \prod f_i = \prod g_i f_i$$

- Path Delay

$$D = P + \sum g_i f_i$$

- Minimized when each stage delay is equal

$$g_i f_i = \hat{h} = \sqrt[N]{H}$$

$$D = P + N \hat{h}$$

$$= P + N \sqrt[N]{H}$$

3 March 2009

26

## Logical Effort

- Work backwards to assign sizing

$$g_i f_i = \sqrt[N]{H}$$


$$f_i = \frac{\sqrt[N]{H}}{g_i}$$

3 March 2009

27

## Logical Effort

- Example

 

$$g=1 \quad g=4/3 \quad g=5/3 \quad g=1 \quad g=5/3$$

$$f=w/10 \quad f=x/w \quad f=y/x \quad f=z/y \quad f=20/z$$

$$G = \prod g_i = 1 \cdot \frac{4}{3} \cdot \frac{5}{3} \cdot 1 \cdot \frac{5}{3} = \frac{100}{27}$$

$$F = \frac{C_{out}}{C_{in}} = \frac{20}{10} = 2$$


$$B = 1$$

$$H = G \times FB = \frac{100}{27} \cdot 2 \cdot 1 = \frac{200}{27}$$

3 March 2009

28

## Logical Effort

 

$$g=1 \quad g=4/3 \quad g=5/3 \quad g=1 \quad g=5/3$$

$$f=w/10 \quad f=x/w \quad f=y/x \quad f=z/y \quad f=20/z$$

$$\hat{h} = \sqrt[N]{H} = \sqrt[5]{\frac{200}{27}} = 1.49$$

$$\hat{h} = g_5 f_5 = \frac{5}{3} \cdot \frac{20}{z} = 1.49 \Rightarrow z = 22.3$$

$$\hat{h} = g_4 f_4 = 1 \cdot \frac{z}{y} = 1.49 \Rightarrow y = 15.0$$

$$\hat{h} = g_3 f_3 = \frac{5}{3} \cdot \frac{y}{x} = 1.49 \Rightarrow x = 16.8$$


$$\hat{h} = g_2 f_2 = \frac{4}{3} \cdot \frac{x}{w} = 1.49 \Rightarrow w = 15.0$$

3 March 2009

29

## Logical Effort

- Example

 

$$G = \prod g_i = 1 \cdot \frac{4}{3} = \frac{4}{3}$$

$$F = \frac{C_{out}}{C_{in}} = \frac{10}{1} = 10$$

$$B = \frac{C_{total}}{C_{useful}} = \frac{2z}{z} = 2$$


$$H = G \times FB = \frac{4}{3} \cdot 10 \cdot 2 = \frac{80}{3}$$

3 March 2009

30

## Logical Effort

- Example (cont)

 

$$\hat{h} = \sqrt[3]{fH} = \sqrt[3]{\frac{80}{3}} = 5.16$$

$$\hat{h} = g_2 f_2 = \frac{4}{3} \cdot \frac{10}{z} = 5.16 \Rightarrow z = 2.58$$