

## Topics

- Power Dissipation
- Technology Scaling

3 March 2009

1

## Where Does Power Go in CMOS?

- Dynamic Power Consumption
  - Charging and discharging capacitors
  - Short circuit currents: short circuit path between supply rails during switching
- Static Power Consumption
  - Leakage: leaking diodes and transistors

3 March 2009

2

## Power dissipation

- Static power dissipation
  - In theory, CMOS has no static power dissipation
  - There is a slight current (sub-threshold leakage current and gate leakage current) on the order of 0.1-0.5nA per device
  - At 5V supply voltage, 0.5-2.5 nW static power dissipation per device
  - Million-gate chip will have 0.5-2.5 mW static power dissipation
  - Billion-gate chip ???

3 March 2009

3

## Power dissipation


- Dynamic power dissipation
  - Proportional to load capacitance and frequency
  - Proportional to square of the supply voltage
    - Reducing supply voltages can effectively reduce dynamic power
    - However, reduced supply voltage will increase delays
    - There is a limit on reduction of supply voltage

3 March 2009

4
 
## Power dissipation

- Dynamic power dissipation
  - Switching causes charging/discharging current flow which will cause power dissipation



3 March 2009

5

## Power dissipation

- Dynamic power dissipation

$$\begin{aligned}
 P &= \frac{1}{T} \left[ \int_0^{T/2} i_n(t) V_{out} dt + \int_{T/2}^T i_p(t) (V_{DD} - V_{out}) dt \right] \\
 &= \frac{1}{T} \left[ -C_L \int_{V_{DD}}^0 V_{out} dV_{out} + C_L \int_0^{V_{DD}} (V_{DD} - V_{out}) dV_{out} \right] \\
 &= \frac{C_L}{T} \left[ \frac{V_{DD}^2}{2} + \frac{V_{DD}^2}{2} \right] \\
 &= C_L V_{DD}^2 f
 \end{aligned}$$

3 March 2009

6

## Power dissipation

- Example

$$V_{DD} = 5V$$

$$f = 1GHz$$

$$C_L = 1pF$$

$$P = C_L V_{DD}^2 f$$


$$= 1pf \cdot 5^2 \cdot 1GHz$$

$$= 25mW$$

3 March 2009

7

## Power dissipation

 

$$P = \alpha C_L V_{DD}^2 f$$

- $\alpha$  is the activity factor - i.e. the probability that a clock event results in a transition

3 March 2009

8

## Power dissipation

- Example: NAND gate with independent and uniformly distributed inputs.
  - Probability of NAND gate outputs:  $P_0=0.25$  and  $P_1=0.75$ .
  - Therefore, probability of  $0 \rightarrow 1$  transition is  $\alpha_{0 \rightarrow 1} = P_0 P_1 = 0.1875$

$$V_{DD} = 5V$$

$$f = 1GHz$$

$$C_L = 1pF$$

$$P = \alpha C_L V_{DD}^2 f$$


$$= 0.1875 \cdot 1pf \cdot 5^2 \cdot 1GHz$$

$$= 4.7mW$$

3 March 2009

9
 
## Modification for Circuits with Reduced Swing



- Can exploit reduced swing to lower power (e.g., reduced bit-line swing in memory)

3 March 2009

10


## Power dissipation

- Short circuit current dissipation
  - Short circuit current occurs when both transistors are "on" temporarily
  - Proportional to the ratio of rise time
  - Since the rise time is usually much less than period  $T$ , it can be usually ignored

3 March 2009

11


## Short Circuit Currents

 

3 March 2009

12

## Minimizing Short-Circuit Power

 


- Keep the input and output rise/fall times the same
- If  $V_{dd} < V_{tn} + |V_{tp}|$  then short-circuit power can be *eliminated!*

3 March 2009

13

## Leakage

 


- Sub-threshold current is one of most difficult issues in low-power circuit design!

3 March 2009

14

## Sub-threshold Leakage Component

 

- Leakage control is critical for low-voltage operation

3 March 2009

15

## Principles for Power Reduction

- The first choice: Reduce voltage!
  - Recent years have seen an acceleration in supply voltage reduction
  - Design at very low voltages still open question
- Reduce switching activity
- Reduce physical capacitance

3 March 2009

16

## Goals of Technology Scaling

- Make things cheaper:
  - Want to sell more functions (transistors) per chip for the same money
  - Build same products cheaper, sell the same part for less money
  - Price of a transistor has to be reduced
  - But also want to be faster, smaller, lower power

3 March 2009

17

## Technology Scaling

- Goals of scaling the dimensions by 30%:
  - Reduce gate delay by 30% (increase operating frequency by 43%)
  - Double transistor density
  - Reduce energy per transition by 30%
- Die size used to increase by 14% per generation
- Technology generation spans 2-3 years

3 March 2009

18

## Technology Scaling Models

- Full Scaling (Constant Electrical Field)
  - ideal model — dimensions and voltage scale together by the same factor  $S$
- Fixed Voltage Scaling
  - most common model until recently — only dimensions scale, voltages remain constant
- General Scaling
  - most realistic for today's situation — voltages and dimensions scale with different factors

3 March 2009

19

## Scaling Relationships for Long Channel Devices

Parameter	Relation	Full Scaling	General Scaling	Fixed Voltage Scaling
$W, L, t_{ox}$		$1/S$	$1/S$	$1/S$
$V_{DD}, V_T$		$1/S$	$1/U$	1
$N_{SUB}$	$V/W_{dop}^2$	$S$	$S^2/U$	$S^2$
Area/Device	$WL$	$1/S^2$	$1/S^2$	$1/S^2$
$C_{ox}$	$1/t_{ox}$	$S$	$S$	$S$
$C_L$	$C_{ox}WL$	$1/S$	$1/S$	$1/S$
$k_n, k_p$	$C_{ox}W/L$	$S$	$S$	$S$
$I_{av}$	$k_n \mu V^2$	$1/S$	$S/U^2$	$S$
$t_p$ (intrinsic)	$C_L V / I_{av}$	$1/S$	$U/S^2$	$1/S^2$
$P_{av}$	$C_L V^2 / t_p$	$1/S^2$	$S/U^3$	$S$
PDP	$C_L V^2$	$1/S^3$	$1/SU^2$	$1/S$

3 March 2009

20

## Technology Evolution (2000 data)

- International Technology Roadmap for Semiconductors (ITRS)


Year of Introduction	1999	2000	2001	2004	2008	2011	2014
Technology node [nm]	180	150	130	90	60	40	30
Supply [V]	1.5-1.8	1.5-1.8	1.2-1.5	0.9-1.2	0.6-0.9	0.5-0.6	0.3-0.6
Wiring levels	6-7	6-7	7	8	9	9-10	10
Max frequency [GHz]_Local-Global	1.2	1.6-1.4	2.1-1.6	3.5-2	7.1-2.5	11-3	14.9 -3.6
Max $\mu P$ power [W]	90	106	130	160	171	177	188
Bat. power [W]	1.4	1.7	2.0	2.4	2.1	2.3	2.5

Node years: 2007/65nm, 2010/45nm, 2013/32nm, 2016/23nm

3 March 2009

21


## Technology Scaling (1)

 

3 March 2009

22

## Technology Scaling (2)

 


$t_p$  decreases by 13%/year  
50% every 5 years!

3 March 2009

23


## Technology Scaling (3)

 

3 March 2009

24


## Technology Scaling (4)

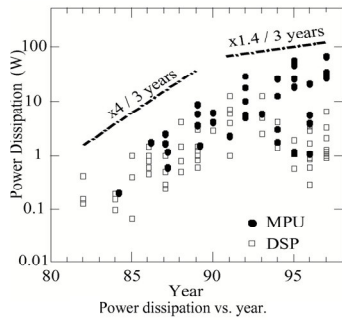

3 March 2009

25

## μProcessor Scaling

 


P. Gelsinger; μProcessors for the New Millennium, ISSCC 2001

3 March 2009

26

## μProcessor Power

 

P. Gelsinger; μProcessors for the New Millennium, ISSCC 2001

3 March 2009

27

## Processor Technology Challenges

- Power dissipation
  - Pentium 4W/cm<sup>2</sup>
  - Hot plate 10W/cm<sup>2</sup>
  - Pentium II 20W/cm<sup>2</sup>,
  - Pentium III 50W/cm<sup>2</sup>
  - Nuclear reactor 200W/cm<sup>2</sup>

(Source: S. Borkar, IEEE Micro 1999)
- Design variations
  - PTV variations (process parameters, temperature and voltages including threshold voltages)
- Wire delays
  - Clock network, memory bandwidth

3 March 2009

28

## 2010 Outlook

- Performance 2X/16 months
  - 1 TIP (terra instructions/s)
  - 30 GHz clock
- Size
  - No of transistors: 2 Billion
  - Die: 40\*40 mm
- Power
  - 10kW!!
  - Leakage: 1/3 active Power

3 March 2009

29