

# VLSI Design Verification and Testing

## Combinational ATPG

Mohammad Tehranipoor  
Electrical and Computer Engineering  
University of Connecticut

27 September 2009

1


# Overview: Major ATPG Algorithms

- Definitions
- D-Algorithm (Roth) -- 1966
  - D-cubes
  - Bridging faults
  - Logic gate function change faults
- PODEM (Goel) -- 1981
  - X-Path-Check
  - Backtracing
- Summary

27 September 2009

2

## Forward Implication

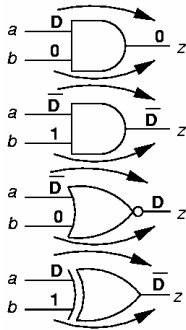

Results in logic gate inputs that are significantly labeled so that output is uniquely determined

AND gate forward implication table:


	b	0	1	X	D	$\bar{D}$
a	0	0	0	0	0	0
	1	0	1	X	D	$\bar{D}$
	X	0	X	X	X	X
	D	0	D	X	D	0
	$\bar{D}$	0	$\bar{D}$	X	0	$\bar{D}$

27 September 2009

3
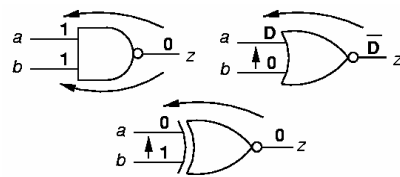
## Backward Implication

Unique determination of all gate inputs when the gate output and some of the inputs are given



27 September 2009

4

## Implication Stack


- Push-down stack. Records:
  - Each signal set in circuit by ATPG
  - Whether alternate signal value already tried
  - Portion of binary search tree already searched

Stack ptr.	Signal	Value	Alternative tried
	A	1	NO
	C	1	NO
	E	1	NO
	B	0	YES

27 September 2009

5
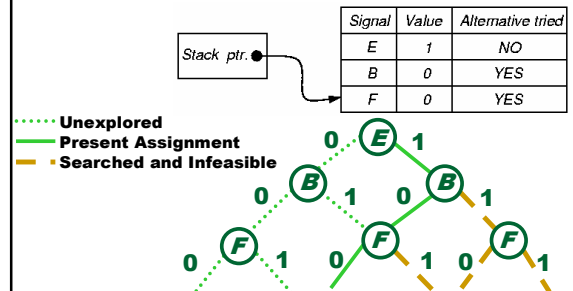
## Implication Stack, Decision Tree, and Backtrack



27 September 2009

6

## Objectives and Backtracing in ATPG

- **Objective** – desired signal value goal for ATPG
  - Guides it away from infeasible/hard solutions
  - Uses heuristics
    - E.g. which fault site to choose first?
- **Backtrace** – Determines which primary input and value to set to achieve objective
  - Use heuristics such as nearest PI
- **Forward trace** – Determines gate through which the fault effect should be sensitized
  - Use heuristics selecting output that is closest to the present fault effect

27 September 2009

7

## Branch-and-Bound Search

- Efficiently searches binary search tree
- **Branching** – At each tree level, selects which input variable to set to what value
- **Bounding** – Avoids exploring large tree portions by artificially restricting search decision choices
  - Complete exploration is impractical
  - Uses *heuristics*
- **Example:**
  - For a circuit with inputs  $A, B, C, D$  and  $E: \bar{A}\bar{B}...$  does not achieve objective.

27 September 2009

8

## D-Algorithm – Roth (1966)


- **Fundamental concepts invented:**
  - First complete ATPG algorithm
  - **D-Cube**
  - **D-Calculus**
  - **Implications** – forward and backward
  - **Implication stack**
  - **Backtrack**
  - Test Search Space

27 September 2009

9
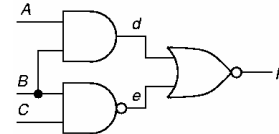
## Singular Cover - Example

- Minimal set of logic signal assignments to represent a function
  - Show *prime implicants and prime implicates of Karnaugh map (with explicitly showing the outputs too)*



Gate	Inputs	Output	Gate	Inputs	Output
AND	A B	d	NOR	d C	F
1	0 X	0	1	1 X	0
2	X 0	0	2	X 1	0
3	1 1	1	3	0 0	1

27 September 2009

10

## D-Cube - Example

- Collapsed truth table entry to characterize logic
- Use Roth's 5-valued algebra
- Can change all  $D$ 's to  $\bar{D}$ 's and  $\bar{D}$ 's to  $D$ 's (do both)
- AND gate:

	A	B	d
Rows 3 & 1	$\bar{D}$	1	$\bar{D}$
Reverse inputs	1	$\bar{D}$	$\bar{D}$
AND two cubes	$\bar{D}$	$\bar{D}$	$\bar{D}$
Interchange $D$ and $\bar{D}$	1	$\bar{D}$	$\bar{D}$
	$\bar{D}$	1	$\bar{D}$

AND Gate Propagation D-Cubes

27 September 2009

11

## D-Cube Operation of D-Intersection

- $\psi$  – undefined (same as  $\phi$ )
- $\mu$  or  $\lambda$  – requires inversion of  $D$  and  $\bar{D}$
- **D-intersection:**

$$0 \cap 0 = 0 \cap X = X \cap 0 = 0$$

$$1 \cap 1 = 1 \cap X = X \cap 1 = 1$$

$$X \cap X = X$$

- **D-containment** –  
Cube  $a$  contains  
Cube  $b$  if  $b$  is a  
subset of  $a$

$\cap$	0	1	X	D	$\bar{D}$
0	0	$\phi$	0	$\psi$	$\psi$
1	$\phi$	1	1	$\psi$	$\psi$
X	0	1	X	D	$\bar{D}$
$\bar{D}$	$\psi$	$\psi$	D	$\mu$	$\lambda$
D	$\psi$	$\psi$	D	$\lambda$	$\mu$

27 September 2009

12

## Primitive D-Cube of Failure (PDF)

- Models circuit faults:
  - *Stuck-at-0*
  - *Stuck-at-1*
  - Other faults, such as *Bridging fault* (short circuit)
  - Arbitrary change in logic function
- AND Output sa0: "1 1 D"
- AND Output sa1: "0 X  $\bar{D}$ "  
"X 0  $\bar{D}$ "
- Wire sa0: "D"
- *Propagation D-cube* – models conditions under which fault effect propagates through gate

27 September 2009

15


## Implication Procedure

1. Model fault with appropriate *primitive D-cube of failure* (PDF)
2. Select *propagation D-cubes* to propagate fault effect to a circuit output (*D-drive* procedure)
3. Select *singular cover* cubes to justify internal circuit signals (*Consistency* procedure)
  - Put signal assignments in *test cube*
  - Regrettably, cubes are selected very arbitrarily by D-ALG

27 September 2009

14

## Bridging Fault Circuit

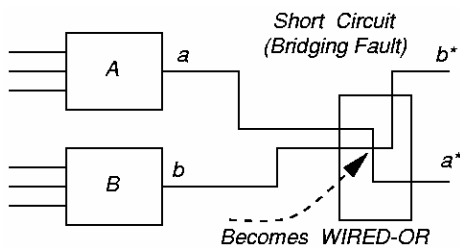

27 September 2009

15

## Construction of Primitive D-Cubes of Failure

1. Make cube set  $\alpha 1$  when good machine output is 1 and set  $\alpha 0$  when good machine output is 0
2. Make cube set  $\beta 1$  when failing machine output is 1 and  $\beta 0$  when it is 0
3. Change  $\alpha 1$  outputs to 0 and D-intersect each cube with every  $\beta 0$ . If intersection works, change output of cube to D
4. Change  $\alpha 0$  outputs to 1 and D-intersect each cube with every  $\beta 1$ . If intersection works, change output of cube to  $\bar{D}$

27 September 2009

16


## Bridging Fault D-Cubes of Failure

Cube-set	a	b	a*	b*	Cube-set	a	b	a*	b*
$\alpha 0$	0	X	0	X	PDFs for Bridging fault	1	0	1	$\bar{D}$
	X	0	X	0					
$\alpha 1$	1	X	1	X					
	X	1	X	1					
$\beta 0$	0	0	0	0					
$\beta 1$	X	1	1	1					
	1	X	1	1					

27 September 2009

17
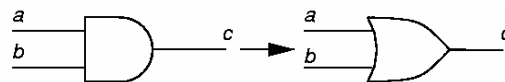
## Gate Function Change D-Cube of Failure



Cube-set	a	b	c	Cube-set	a	b	c
$\alpha 0$	0	X	0	PDFs for AND changing to OR	0	1	$\bar{D}$
	X	0	0				
$\alpha 1$	1	1	1				
$\beta 0$	0	0	0				
$\beta 1$	1	X	1				
	X	1	1				

27 September 2009

18

## Propagation D-Cube

- Collapsed truth table entry to characterize logic
- Use Roth's 5-valued algebra
- AND gate: use the rules given earlier using  $\alpha$  and  $\beta$  but in this case work with good circuit only

Write all primitive Cubes of AND gate and then create propagation cubes	A	B	d
	D	1	D
	1	D	D
	D	D	D
	$\bar{D}$	$\bar{D}$	$\bar{D}$
	1	$\bar{D}$	$\bar{D}$
	$\bar{D}$	1	$\bar{D}$
	$\bar{D}$	$\bar{D}$	$\bar{D}$

27 September 2009

19

## D-Algorithm – Top Level

- Number all circuit lines in increasing level order from PIs to POs;
- Select a primitive D-cube of the fault to be the *test cube*;
  - Put logic outputs with inputs labeled as D ( $\bar{D}$ ) onto the *D-frontier*;
- D-drive* ();
- Consistency* ();
- return ();

27 September 2009

20

## D-Algorithm -- D-drive

```

while (untried fault effects on D-frontier)
  select next untried D-frontier gate for propagation;
  while (untried fault effect fanouts exist)
    select next untried fault effect fanout;
    generate next untried propagation D-cube;
    D-intersect selected cube with test cube;
    if (intersection fails or is undefined) continue;
    if (all propagation D-cubes tried & failed) break;
    if (intersection succeeded)
      add propagation D-cube to test cube -- recreate D-frontier;
      Find all forward & backward implications of assignment;
      save D-frontier, algorithm state, test cube, fanouts, fault;
      break;
    else if (intersection fails & D and  $\bar{D}$  in test cube) Backtrack ();
    else if (intersection fails) break;
  - if (all fault effects unpropagatable) Backtrack ();
    
```

27 September 2009

21

## D-Algorithm -- Consistency

```

g = coordinates of test cube with 1's & 0's;
if (g is only PIs) fault testable & stop;
for (each unjustified signal in g)
  Select highest # unjustified signal z in g, not a PI;
  if (inputs to gate z are both D and  $\bar{D}$ ) break;
  while (untried singular covers of gate z)
    select next untried singular cover;
    if (no more singular covers)
      If (no more stack choices) fault untestable & stop;
      else if (untried alternatives in Consistency)
        pop implication stack -- try alternate assignment;
      else
        Backtrack ();
        D-drive ();
  If (singular cover D-intersects with z) delete z from g, add
  inputs to singular cover to g, find all forward and backward
  implications of new assignment, and break;
  If (intersection fails) mark singular cover as failed;
    
```

27 September 2009

22

## Backtrack


```

if (PO exists with fault effect) Consistency ();
else pop prior implication stack setting to try alternate
assignment;
if (no untried choices in implication stack)
  fault untestable & stop;
else return;
    
```

27 September 2009

23

## Circuit Example 7.1 and Truth Table

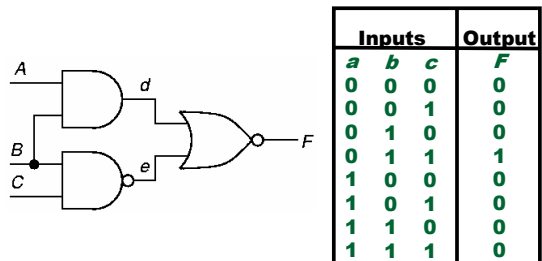


27 September 2009

24


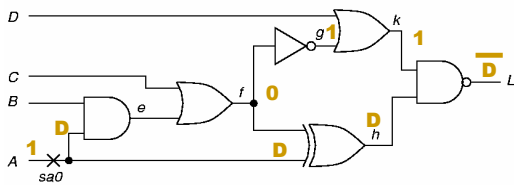
## Step 5 -- Example 7.2

- Step 5 – **Consistency** –  $f = 0$  Already set




27 September 2009

31
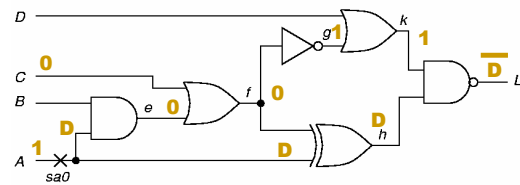
## Step 6 -- Example 7.2

- Step 6 – **Consistency** – Set  $c = 0$ , Set  $e = 0$




27 September 2009

32
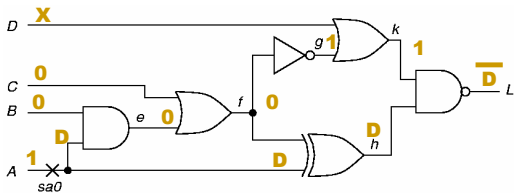
## D-Chain Dies -- Example 7.2

- Step 7 – **Consistency** – Set  $B = 0$
- D-Chain** dies




- Test cube:  $A, B, C, D, e, f, g, h, k, L$

27 September 2009

33

## Example 7.3 – Fault $s_{sa1}$

- Primitive D-cube of Failure

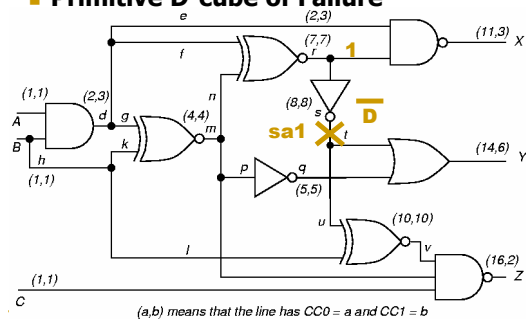


(a,b) means that the line has  $CC0 = a$  and  $CC1 = b$

27 September 2009

34

## Example 7.3 – Step 2 $s_{sa1}$

- Propagation D-cube for  $v$

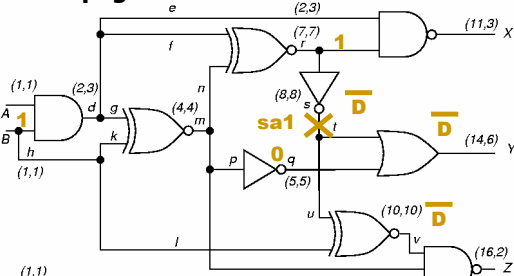


(a,b) means that the line has  $CC0 = a$  and  $CC1 = b$

27 September 2009

35

## Example 7.3 – Step 2 $s_{sa1}$

- Forward & Backward Implications

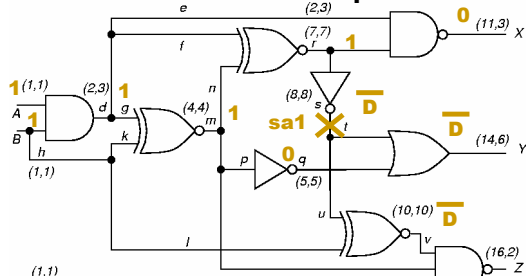


(a,b) means that the line has  $CC0 = a$  and  $CC1 = b$

27 September 2009

36

### Example 7.3 – Step 3 $s$ sa1

#### ■ Propagation D-cube for $Z$ -test

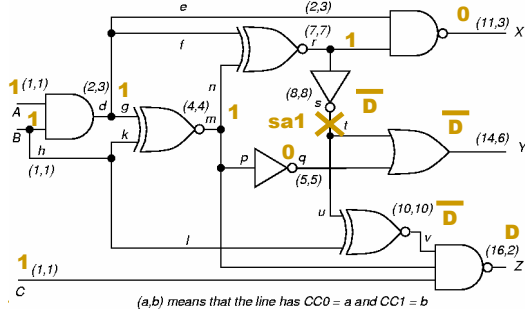


27 September 2009

37

### Example 7.3 – Fault $u$ sa1

#### ■ Primitive D-cube of Failure

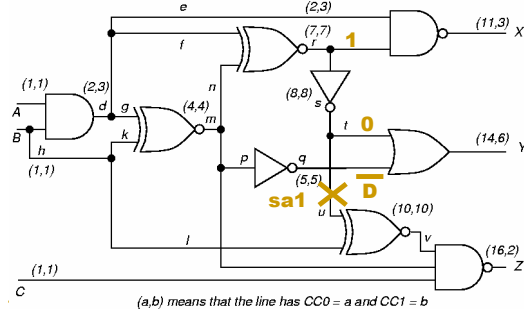


27 September 2009

38

### Example 7.3 – Step 2 $u$ sa1

#### ■ Propagation D-cube for $v$

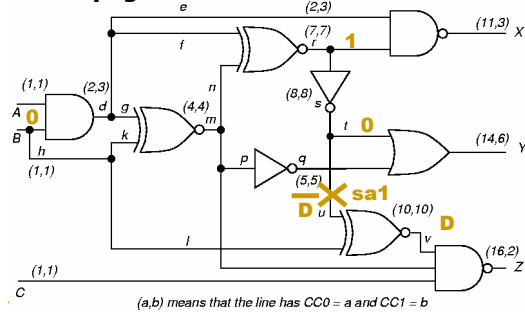


27 September 2009

39

### Example 7.3 – Step 2 $u$ sa1

#### ■ Forward and backward implications

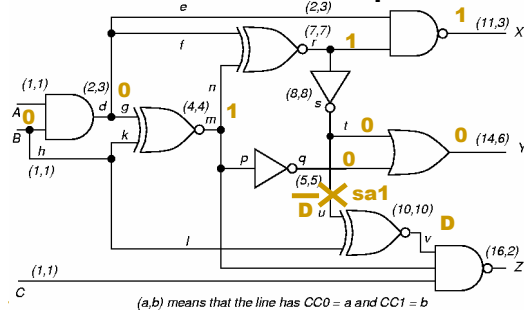

27 September 2009

40

### Inconsistent


- $d = 0$  and  $m = 1$  cannot justify  $r = 1$  (equivalence)
  - Backtrack
  - Remove  $B = 0$  assignment

27 September 2009

41

### Example 7.3 – Backtrack
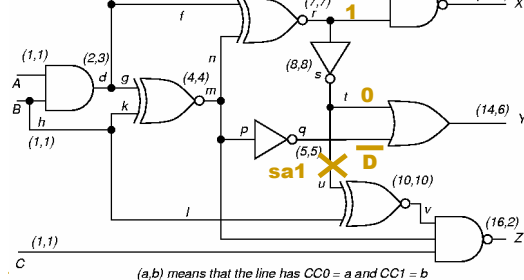
#### ■ Need alternate propagation D-cube for $v$




27 September 2009

42

### Example 7.3 – Step 3 $\cup$ sa1

#### ■ Propagation D-cube for $v$

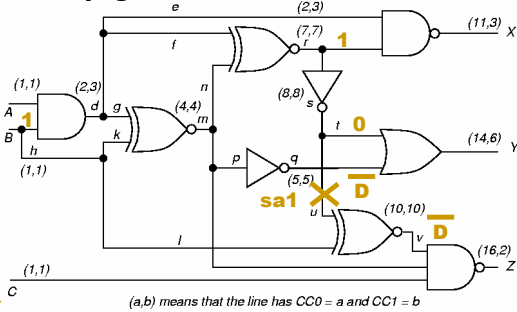


27 September 2009

43

### Example 7.3 – Step 4 $\cup$ sa1

#### ■ Propagation D-cube for $Z$

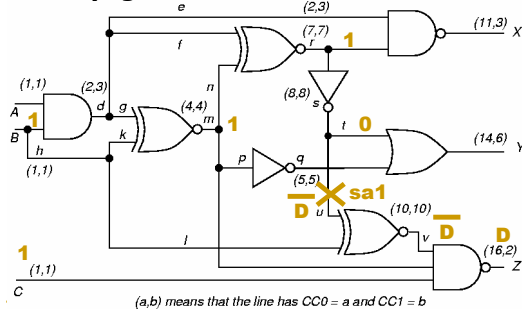


27 September 2009

44

### Example 7.3 – Step 4 $\cup$ sa1
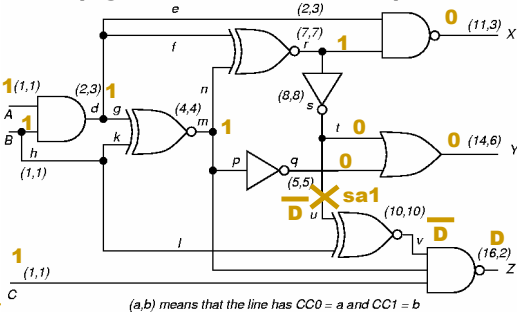
#### ■ Propagation D-cube for $Z$ and implications



27 September 2009

45

### PODEM\* -- Goel (1981)

- **New concepts introduced:**
  - Expand binary decision tree only around primary inputs
  - Use **X-PATH-CHECK** to test whether **D-frontier** still there
  - **Objectives** -- bring ATPG closer to propagating **D (D)** to PO
  - **Backtracing**

\* Path Oriented DEcision Making

27 September 2009

46

### Motivation

- IBM introduced semiconductor DRAM memory into its mainframes – late 1970's
- Memory had error correction and translation circuits – improved reliability
  - D-ALG unable to test these circuits
    - Search too undirected
    - Large XOR-gate trees
    - Must set all external inputs to define output
  - Needed a better ATPG tool

27 September 2009

47

### PODEM High-Level Flow

1. Assign binary value to unassigned PI
2. Determine implications of all PIs
3. Test Generated? If so, **done**.
4. Test possible with more assigned PIs? If maybe, go to **Step 1**
5. Is there untried combination of values on assigned PIs? If not, **exit: untestable fault**
6. Set untried combination of values on assigned PIs using objectives and backtrace. Then, go to **Step 2**

27 September 2009

48



### Example 7.3 Again

- Select path  $s - Y$  for fault propagation

$(a,b)$  means that the line has  $CC0 = a$  and  $CC1 = b$

27 September 2009 49

### Example 7.3 -- Step 2 $s$ sa1

- Initial objective: Set  $r$  to 1 to excite fault

$(a,b)$  means that the line has  $CC0 = a$  and  $CC1 = b$

27 September 2009 50

### Example 7.3 -- Step 3 $s$ sa1

- Backtrace from  $r$

$(a,b)$  means that the line has  $CC0 = a$  and  $CC1 = b$

27 September 2009 51

### Example 7.3 -- Step 4 $s$ sa1

- Set  $A = 0$  in implication stack

$(a,b)$  means that the line has  $CC0 = a$  and  $CC1 = b$

27 September 2009 52

### Example 7.3 -- Step 5 $s$ sa1

- Forward implications:  $d = 0, X = 1$

$(a,b)$  means that the line has  $CC0 = a$  and  $CC1 = b$







27 September 2009 53







### Example 7.3 -- Step 6 $s$ sa1

- Initial objective: set  $r$  to 1

$(a,b)$  means that the line has  $CC0 = a$  and  $CC1 = b$

27 September 2009 54

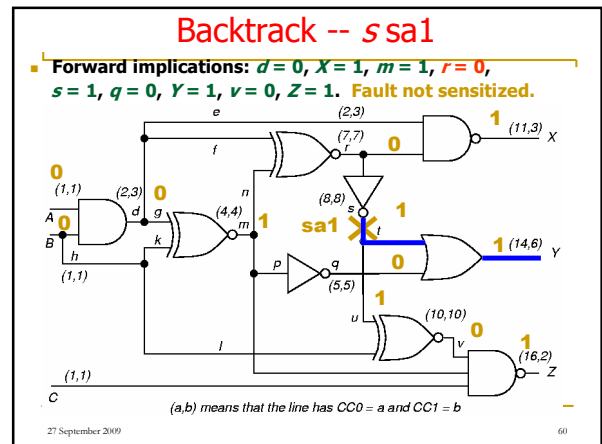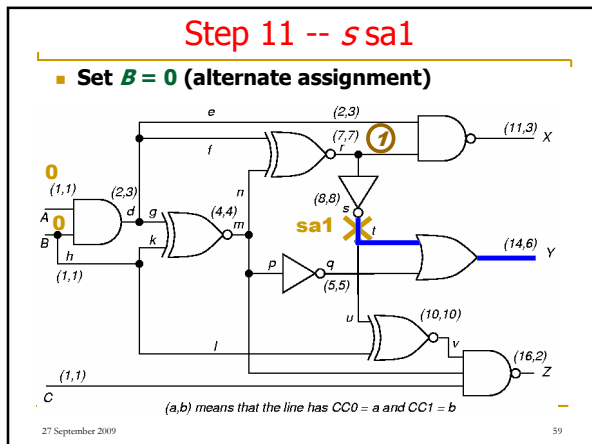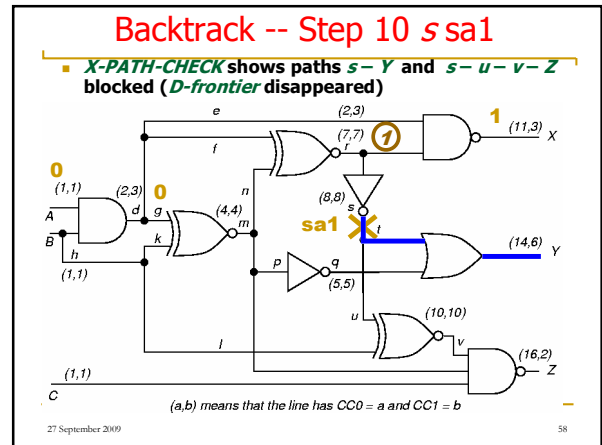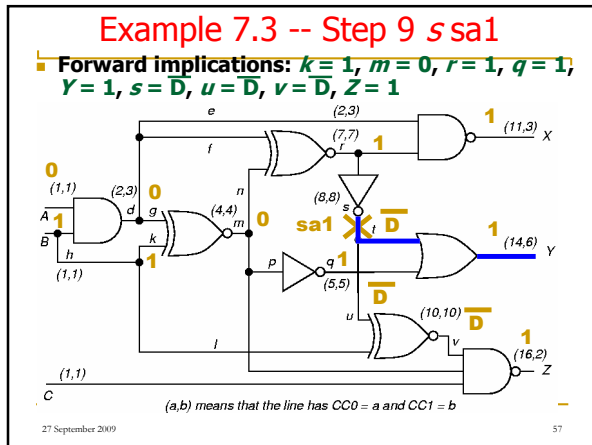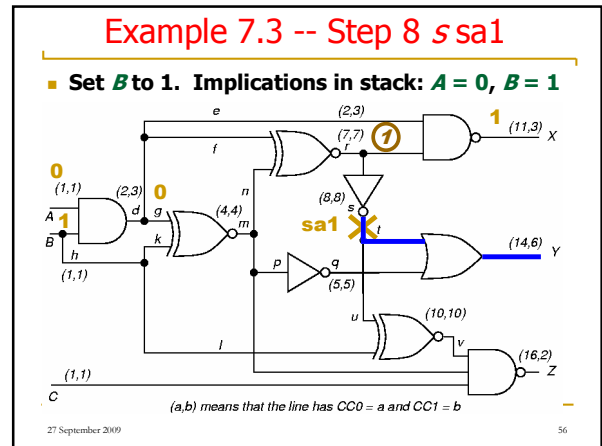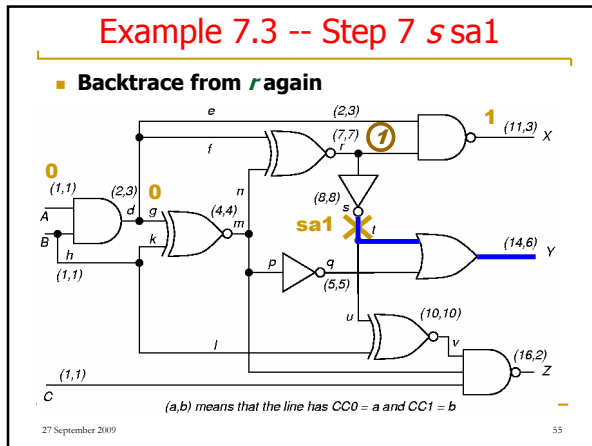

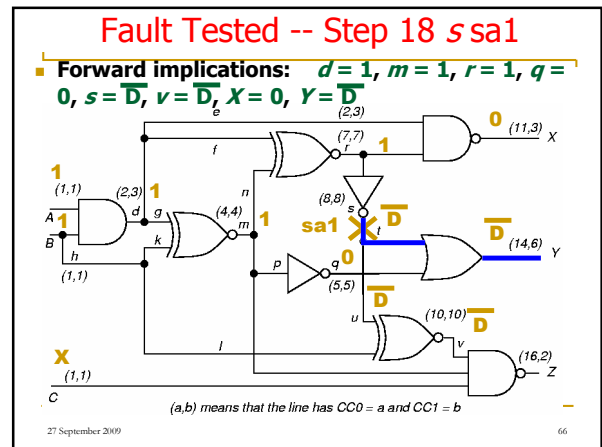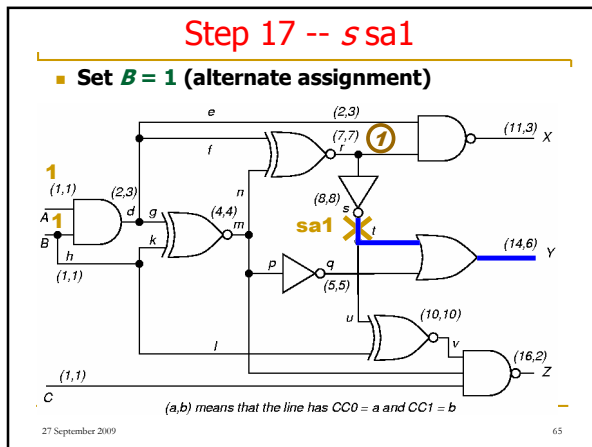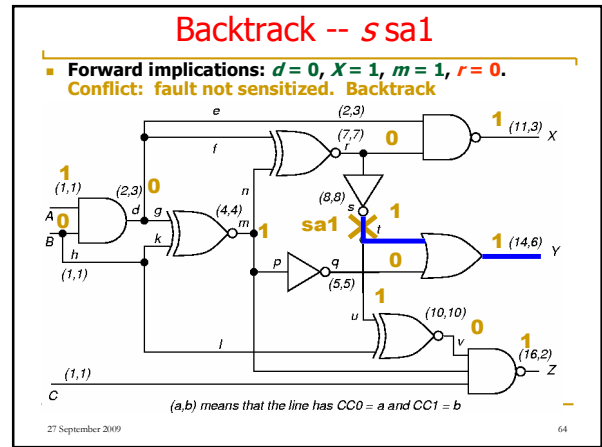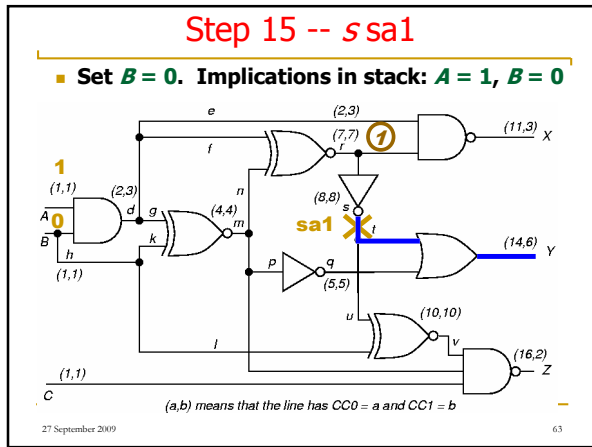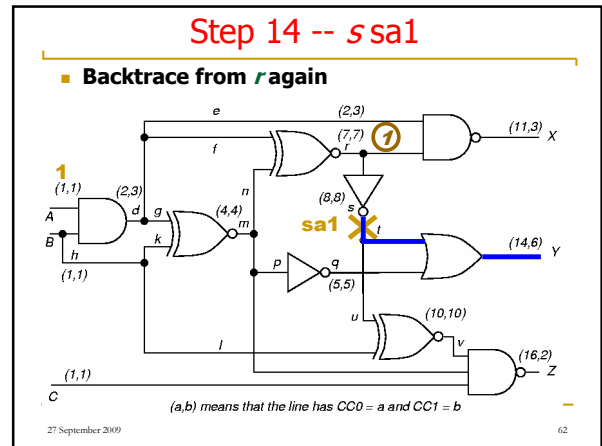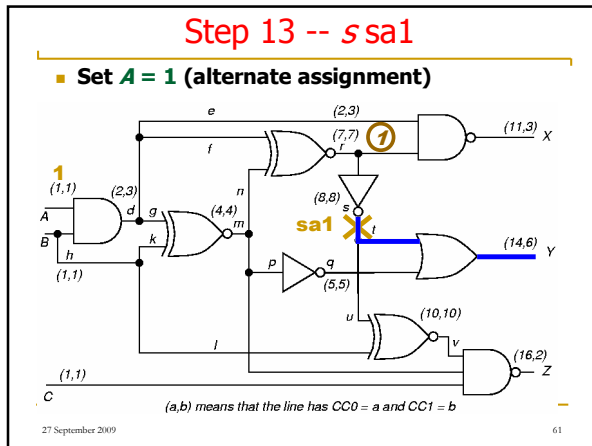

## Backtrace ( $s, v_s$ ) Pseudo-Code

```
 $v = v_s$ ;  
while ( $s$  is a gate output)  
  if ( $s$  is NAND or INVERTER or NOR)  $v = \bar{v}$ ;  
  if (objective requires setting all inputs)  
    select unassigned input  $a$  of  $s$  with hardest  
    controllability to value  $v$ ;  
  else  
    select unassigned input  $a$  of  $s$  with easiest  
    controllability to value  $v$ ;  
   $s = a$ ;  
return ( $s, v$ ) /* Gate and value to be assigned  
*/;
```

27 September 2009

67

## Objective Selection Code

```
if (gate  $g$  is unassigned) return ( $g, \bar{v}$ );  
select a gate  $P$  from the D-frontier;  
select an unassigned input  $l$  of  $P$ ;  
if (gate  $g$  has controlling value)  
   $c =$  controlling input value of  $g$ ;  
else if (0 value easier to get at input of  
  XOR/EQUIV gate)  
   $c = 1$ ;  
else  $c = 0$ ;  
return ( $l, \bar{c}$ );
```

27 September 2009

68

## PODEM Algorithm

```
while (no fault effect at POs)  
  if ( $xpathcheck$  (D-frontier))  
    ( $l, v_l$ ) =  $Objective$  ( $fault, v_{fault}$ );  
    ( $p_i, v_{p_i}$ ) =  $Backtrace$  ( $l, v_l$ );  
     $Imply$  ( $p_i, v_{p_i}$ );  
    if ( $PODEM$  ( $fault, v_{fault}$ ) == SUCCESS) return (SUCCESS);  
    ( $p_i, v_{p_i}$ ) =  $Backtrack$  ();  
     $Imply$  ( $p_i, v_{p_i}$ );  
    if ( $PODEM$  ( $fault, v_{fault}$ ) == SUCCESS) return (SUCCESS);  
     $Imply$  ( $p_i, "X"$ );  
    return (FAILURE);  
  else if (implication stack exhausted)  
    return (FAILURE);  
  else  $Backtrack$  ();  
return (SUCCESS);
```

27 September 2009

69

## Summary

- D-ALG – First complete ATPG algorithm
  - *D-Cube*
  - *D-Calculus*
  - *Implications* – forward and backward
  - *Implication stack*
  - *Backup*
- PODEM
  - Expand decision tree only around PIs
  - Use *X-PATH-CHECK* to see if *D-frontier* exists
  - *Objectives* -- bring ATPG closer to getting  $D$  ( $\bar{D}$ ) to PO
  - *Backtracing*

27 September 2009

70