

VLSI Design Verification and Testing

I_{DDQ} Current Testing

Mohammad Tehranipoor
Electrical and Computer Engineering
University of Connecticut

23 April 2007

1

Overview

- History and motivation
- Basic principle
- Faults detected by I_{DDQ} tests
- Instrumentation difficulties
- Sematech study
- Limitations of I_{DDQ} testing
- Summary

23 April 2007

2


Motivation

- Early 1990's – Fabrication Line had 50 to 1000 *defects per million (dpm)* chips
 - IBM wants to get 3.4 *defects per million (dpm)* chips (0 defects, 6 σ)
- Conventional way to reduce defects:
 - Increasing test fault coverage
 - Increasing burn-in coverage
 - Increase *Electro-Static Damage* awareness
- New way to reduce defects:
 - I_{DDQ} Testing – also useful for *Failure Effect Analysis*

23 April 2007

3

Basic Principle of I_{DDQ} Testing

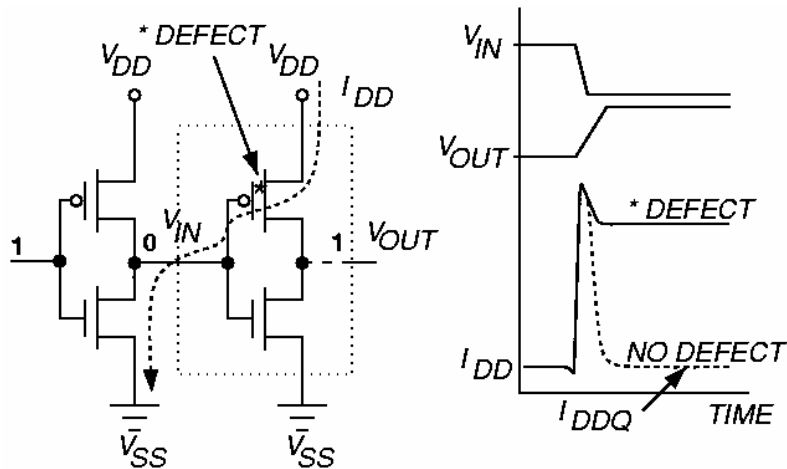

- Measure I_{DDQ} current through V_{SS} bus

23 April 2007

4

Faults Detected by I_{DDQ} Tests

23 April 2007

5

Stuck-at Faults Detected by I_{DDQ} Tests


- *Bridging faults* with stuck-at fault behavior
 - Levi – Bridging of a logic node to V_{DD} or V_{SS} – few of these
 - *Transistor gate oxide short* of 1 K Ω to 5 K Ω
- Floating MOSFET gate defects – do not fully turn off transistor

23 April 2007

6

NAND Open Circuit Defect – Floating gate

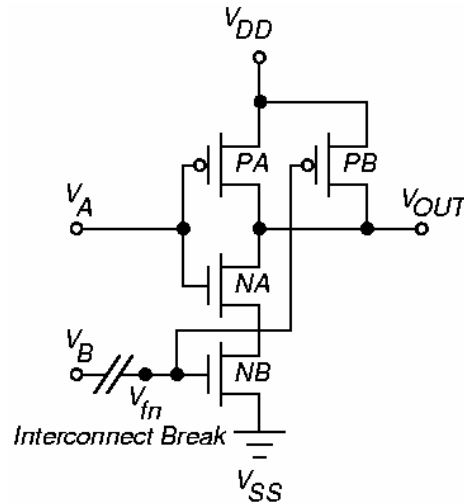- The fault manifests as stuck-at, weak ON for N-FET, or delay fault. Some manifestations can be tested by I_{DDQ} tests



23 April 2007

7

Floating Gate Defects


- Small break in logic gate inputs (100 – 200 Angstroms) lets wires couple by electron tunneling
 - Delay fault and I_{DDQ} fault
- Large open results in stuck-at fault – not detectable by I_{DDQ} test

23 April 2007

8

Bridging Faults $S_1 - S_5$

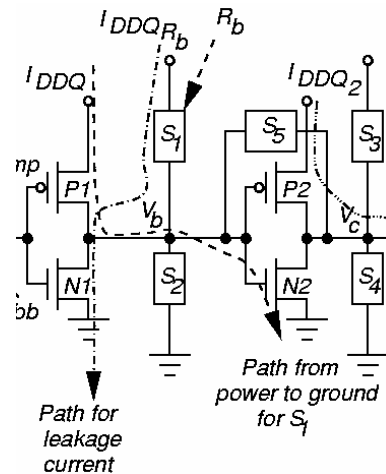- Caused by absolute short ($< 50 \Omega$) or higher R
- Segura *et al.* evaluated testing of bridges with 3 CMOS inverter chain
- I_{DDQRb} tests fault when
 - $R_b > 50 \text{ K}\Omega$ or
 - $0 \leq R_b \leq 100 \text{ K}\Omega$
- Largest deviation when $V_{in} = 5 \text{ V}$
bridged nodes at opposite logic values




23 April 2007

9

$S1 I_{DDQ}$ Depends on K, R_b

K is ratio of width of $n2$ v/s $n1$

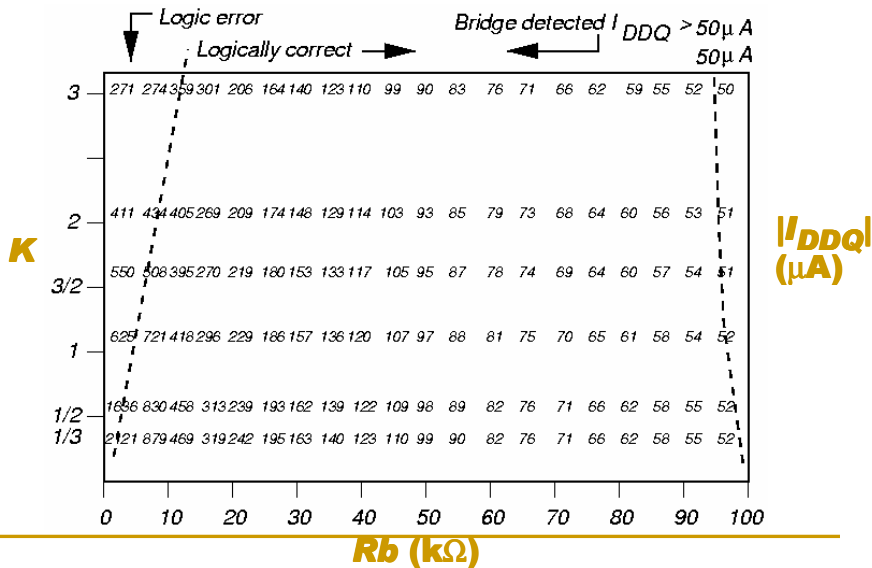

23 April 2007

10

Delay Faults

- Most random CMOS defects cause a timing delay fault, not catastrophic failure
- Many delay faults detected by I_{DDQ} test – late switching of logic gates keeps I_{DDQ} elevated
- Delay faults not detected by I_{DDQ} test
 - Resistive via fault in interconnect
 - Increased transistor threshold voltage fault

23 April 2007

11

Leakage Faults

- Gate oxide shorts cause leaks between gate & source or gate & drain

Weak Faults


- n FET passes logic 1 as $5\text{ V} - V_{tn}$
- p FET passes logic 0 as $0\text{ V} + |V_{tp}|$
- *Weak fault* – one device in C-switch does not turn on
 - Causes logic value degradation in C-switch

23 April 2007

12

Transistor Stuck-Closed Faults

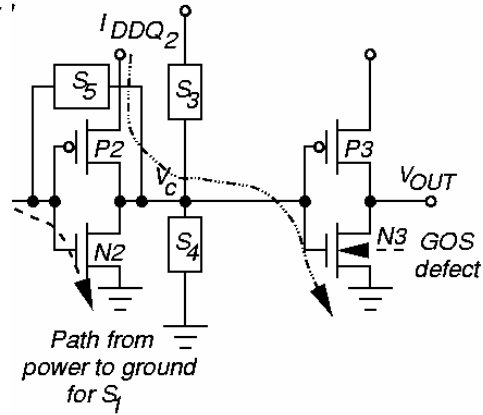
- Due to *gate oxide short* (GOS)
- k = distance of short from drain
- R_S = short resistance
- I_{DDQ2} current results show 3 or 4 orders of magnitude elevation



23 April 2007

13


Gate Oxide Short

 

23 April 2007

14


Logic / I_{DDQ} Testing Zones

 

23 April 2007

15

Fault Coverages for I_{DDQ} Fault Models

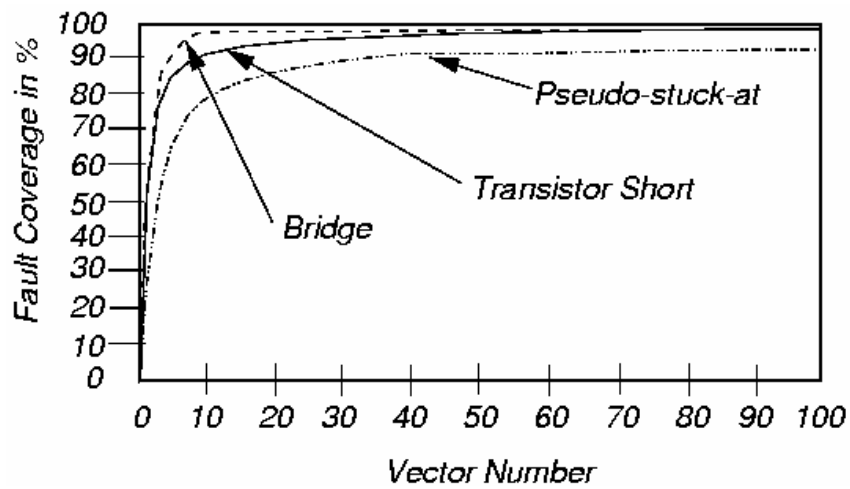

23 April 2007

16

Instrumentation Problems

- Need to measure $< 1 \mu\text{A}$ current at clock $> 10 \text{ kHz}$
- Off-chip I_{DDQ} measurements degraded
 - Pulse width of CMOS IC transient current
 - Impedance loading of tester probe
 - Current leakages in tester
 - High noise of tester load board
- Much slower rate of current measurement than voltage measurement

23 April 2007

17

Sematech Study

- IBM Graphics controller chip – CMOS ASIC, 166,000 standard cells
- $0.8 \mu\text{m}$ static CMOS, $0.45 \mu\text{m}$ Lines (L_{eff}), 40 to 50 MHz Clock, 3 metal layers, 2 clocks
- Full boundary scan on chip
- Tests:
 - Scan flush – 25 ns latch-to-latch delay test
 - 99.7 % scan-based stuck-at faults (slow 400 ns rate)
 - 52 % SAF coverage functional tests (manually created)
 - 90 % transition delay fault coverage tests
 - 96 % pseudo-stuck-at fault cov. I_{DDQ} Tests

23 April 2007

18

Sematech Results

- Test process: Wafer Test → Package Test
 → Burn-In & Retest → Characterize & Failure Analysis
- Data for devices failing some, but not all, tests.

		IDDQ (5 μA limit)					
		pass	pass	fail	fail		
Scan-based Stuck-at	pass		6	1463	7	pass	
	fail	14	0	34	1	pass	
	pass	6	1	13	8	fail	
	fail	52	36	1251		fail	
		pass	fail	pass	fail		
Functional							

23 April 2007

19

Sematech Conclusions

- Hard to find point differentiating good and bad devices for I_{DDQ} & delay tests
- High # passed functional test, failed all others
- High # passed all tests, failed $I_{DDQ} > 5 \mu A$
- Large # passed stuck-at and functional tests
 - Failed delay & IDDQ tests
- Large # failed stuck-at & delay tests
 - Passed I_{DDQ} & functional tests
- Delay test caught delays in chips at higher Temperature burn-in – chips passed at lower T.

23 April 2007

20

Limitations of I_{DDQ} Testing

- Sub-micron technologies have increased leakage currents
 - Transistor sub-threshold conduction
 - Harder to find I_{DDQ} threshold separating good & bad chips
- I_{DDQ} tests work:
 - When average defect-induced current greater than average good IC current
 - Small variation in I_{DDQ} over test sequence & between chips
- Now less likely to obtain two conditions

23 April 2007

21

Summary

- I_{DDQ} tests improve reliability, find defects causing:
 - Delay, bridging, weak faults
 - Chips damaged by electro-static discharge
- No natural breakpoint for current threshold
 - Get continuous distribution – bimodal would be better
- Conclusion: now need stuck-fault, I_{DDQ} and delay fault testing combined
- Still uncertain whether I_{DDQ} tests will remain useful as chip feature sizes shrink further

23 April 2007

22