

# VLSI Design Verification and Testing

## Built-In Self-Test (BIST) - 2

Mohammad Tehranipoor  
Electrical and Computer Engineering  
University of Connecticut

23 April 2007

1

## Overview: Logic BIST

- **Motivation**
- ***Built-in Logic Block Observer (BILBO)***
- ***Test / clock systems***
- ***Test / scan systems***
- ***Circular self-test path (CSTP) BIST***
- **Circuit initialization**
- **Test point insertion**
- **Summary**

23 April 2007

2

## Motivation


- **Complex systems with multiple chips demand elaborate logic BIST architectures**
  - *BILBO* and *test / clock* system
    - Shorter test length, more BIST hardware
  - *STUMPS* & *test / scan* systems
    - Longer test length, less BIST hardware
  - *Circular Self-Test Path*
    - Lowest hardware, lower fault coverage
- **Benefits: cheaper system test, Cost: more hardware.**
- **Must modify fully synthesized circuit for BIST to boost fault coverage**
  - Initialization, *test point* hardware

23 April 2007

3
 
## Built-in Logic Block Observer (BILBO)

- **Combined functionality of D flip-flop, *pattern generator*, *response compacter*, & *scan chain***
  - Reset all FFs to 0 by scanning in zeros




23 April 2007

4
 
## Example BILBO Usage

- **SI** – Scan In
- **SO** – Scan Out
- **Characteristic polynomial:**  $1 + x + \dots + x^n$
- **CUTs A and C:** BILBO1 is MISR, BILBO2 is LFSR
- **CUT B:** BILBO1 is LFSR, BILBO2 is MISR




(a) Example test configuration.

23 April 2007

5
 
## BILBO Serial Scan Mode

- **B1 B2 = "00"**
- **Dark lines show enabled data paths**



23 April 2007

6





## Test / Scan Systems


- **STUMPS architecture**
- **Alternative test per scan systems**
- **Advantages and limitations of test/scan systems**

23 April 2007

11
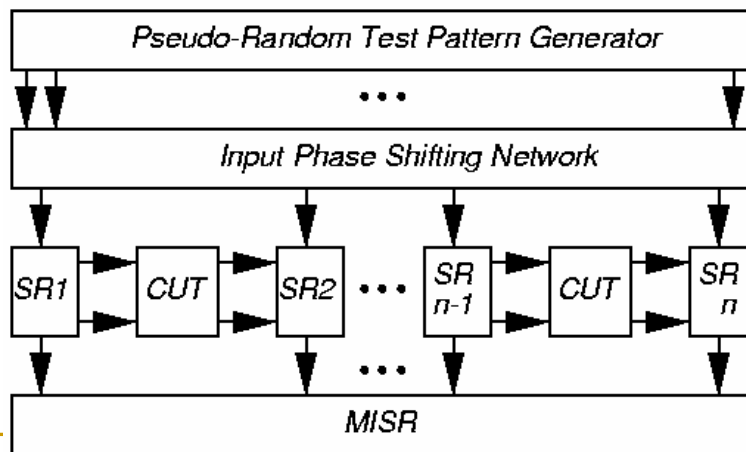
## STUMPS: Architecture and example

- ***SR1 ... SRn*** – 25 full-scan chains, each 200 bits
- **500 chip outputs, need 25 bit MISR (not 5000 bits)**



23 April 2007

12


# STUMPS

- **Test procedure:**
  1. Scan in patterns from LFSR into all scan chains (200 clocks)
  2. Switch to normal functional mode and clock 1 x with system clock
  3. Scan out chains into MISR (200 clocks) where test results are compacted
    - Overlap Steps 1 & 3
- **Requirements:**
  - Every system input is driven by a scan chain
  - Every system output is caught in a scan chain or drives another chip being sampled

23 April 2007

13

## Alternative Test / Scan Systems

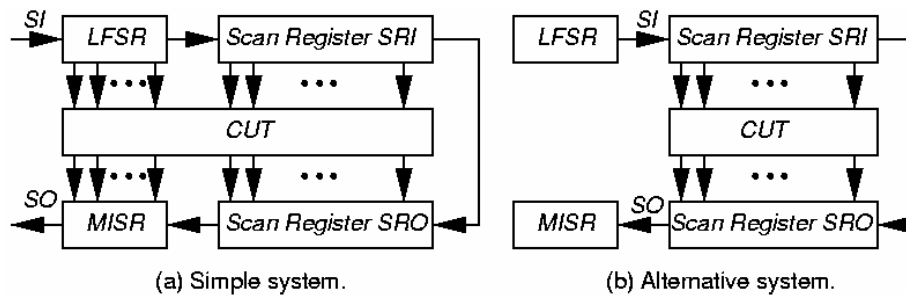

23 April 2007

14

## Test / Scan System

- **New fault tested during 1 clock vector with a complete scan chain shift**
- **Significantly more time required per test than test / clock**
  - **Advantage:** Judicious combination of scan chains and MISR reduces MISR bit width
  - **Disadvantage:** Much longer test pattern set length, causes fault simulation problems
- **Input patterns – time shifted & repeated**
  - Become *correlated* – reduces fault detection effectiveness
  - Use XOR network to phase shift & decorrelate

23 April 2007

15

## BILBO vs. STUMPS vs. ATE

- **LSSD: Level-sensitive scan design**
- **ATE rate: 325 MHz      System clock rate: 1 GHz**
- **$P = \# \text{ patterns}$        $L = \text{max. scan chain length}$**
- **$CP = \text{clock period} = 10^{-9} \text{ s}$**
- **$k = \frac{\text{Self-test speed}}{\text{LSSD tester speed}} = 3.07692$**
- **Test times – BILBO:  $P \times CP$  STUMPS:  $P \times L \times CP$   
ATE:  $P \times L \times CP \times k$** 

**External test & ATE: 307 x longer than BILBO**  
**STUMPS: 100 x longer than BILBO**

  - **Due to extra scan chain shifting**

23 April 2007

16




## Circular Self-Test Path (CSTP) BIST

- **Combine pattern generator and response compacter into a single device**
- **Use synthesized hardware flip-flops configured as a circular shift register**
  - **Non-linear mathematical BIST system**
  - ***Superposition* does not hold**
  - **Flip-flop self-test cell – XOR's  $D$  with  $Q$  state from previous FF in CSTP chain**
- **MISR characteristic polynomial:  $f(x) = x^n + 1$**
- **Hard to compute fault coverage**

23 April 2007

17

## CSTP System

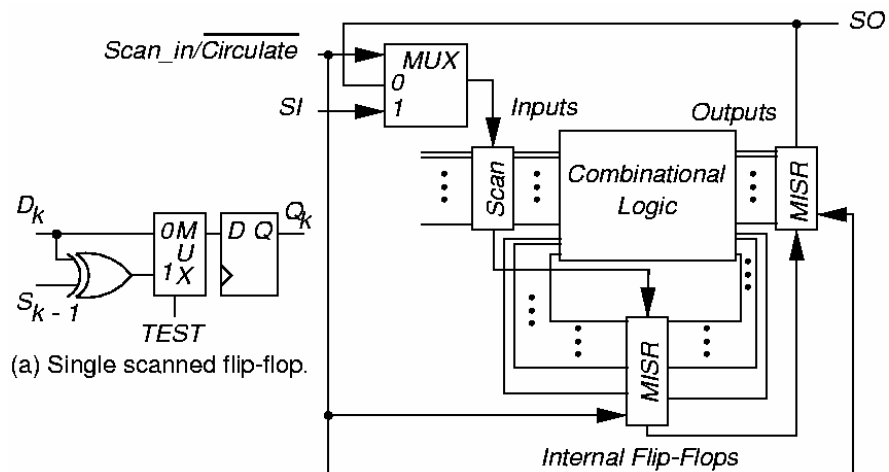

23 April 2007

18

## Examples of CSTP Systems

- **CSTP BIST for 4 ASICs at Lucent Technologies:**
  - Tested everything on 3 of the 4, except for:
    - Input/Output buffers and Input MUX
- **BIST overheads: logic – 20 %, chip area – 13 %**
- **Stuck-at fault coverage – 92 %**

23 April 2007

19

## Circuit Initialization

- **Full-scan BIST – shift in scan chain seed before starting BIST**
- **Partial-scan BIST – critical to initialize all FFs before BIST starts**
  - Otherwise we clock **X**s into MISR and signature is not unique and not repeatable
- **Discover initialization problems by:**
  1. Modeling all BIST hardware
  2. Setting all FFs to **X**s
  3. Running logic simulation of CUT with BIST hardware

23 April 2007

20

## Circuit Initialization (continued)

- If MISR finishes with BIST cycle with **X's** in signature, *Design-for-Testability* initialization hardware must be added
- Add **MS** (*master set*) or **MR** (*master reset*) lines on flip-flops and excite them before BIST starts
- Otherwise:
  1. Break all cycles of FF's
  2. Apply a partial BIST *synchronizing sequence* to initialize all FF's
  3. Turn on the MISR to compact the response

23 April 2007

21

## Isolation from System Inputs

- Must isolate BIST circuits and CUT from normal system inputs during test:
  - *Input MUX*
  - *Blocking gates* –
    - AND gate – apply 0 to 2<sup>nd</sup> AND input, block normal system input
- Note: Neither all of the *Input MUX* nor the *blocking gate* hardware can be tested by BIST
  - Must test externally or with *Boundary Scan* (covered later)

23 April 2007

22

## Test Point Insertion

- **BIST does not detect all faults:**
  - Test patterns not rich enough to test all faults
- **Modify circuit after synthesis to improve signal controllability**
- **Observability addition – Route internal signal to extra FF in MISR or XOR into existing FF in MISR**

23 April 2007

23

## Summary

- **Logic BIST system architecture --**
  - **Advantages:**
    - Higher fault coverage
    - At-speed test
    - Less system test, field test & diagnosis cost
  - **Disadvantage: Higher hardware cost**
- **Architectures: BILBO, test / clock, test / scan**
- **Needs DFT for initialization, and test points**

23 April 2007

24